

**333312 (33)**

BE (3<sup>rd</sup> Semester)

Examination, April-May 2021

Branch : CSE, IT, Mechatronics

**DIGITAL ELECTRONICS & LOGIC  
DESIGN**

*Time Allowed : Three Hours*

*Maximum Marks : 80*

*Minimum Pass Marks : 28*

**Note :** Part (a) is compulsory. Attempt any two parts  
from (b), (c) and (d).

Q. 1. (a) (i) Convert a gray code 1001 1011 into

binary. 1

(ii) Convert  $(3C9A)_{16}$  into decimal. 1

(2)

- (b) Simplify the following Boolean function by using Quine McCluskey method. 7

$$f(A, B, C, D) = \sum m(0, 1, 2, 8, 10, 11, 14, 15)$$

- (c) Simplify following Boolean function using K-map also draw the logic gate circuit. 7

$$f(A, B, C, D) = \sum m(0, 2, 3, 5, 6, 7, 8, 9) \\ + d(10, 11, 12, 13, 14, 15)$$

- (d) Simplify Boolean function in sum of product.

(i)  $(X+Z) (Z\bar{Y}+XZ) (\bar{X}Z+\bar{Y})$  4

(ii)  $[A\bar{B}(C+BD)+\bar{A}\bar{B}]C$  3

- Q. 2. (a) Explain Demux. 2

- (b) Design a BCD to Excess 3 code converter using AND, OR, EXOR. 7

333312 (33)

(3)

(c) Implement the following Boolean function using 4 : 1 MUX. 7

$$f(A, B, C, D) = \sum m(0, 1, 2, 4, 6, 9, 12, 14)$$

(d) Explain BCD adder with diagram. 7

Q. 3. (a) What do you mean by flip flop? 2

(b) Convert SR FF into JK. Also draw logic diagram. 7

(c) Draw the circuit of RTL using NOR gate & explain it. 7

(d) Explain race around condition in JK F/F. Suggest a suitable modification in JK F/F to overcome this problem. 7

Q. 4. (a) Write two applications of shift register. 2

(b) Explain shift register with its classifications. 7

(c) Design divide by 6 counter using T F/F. Write state table & reduce the expression using K Map. Also draw logic diagram. 7

(4)

(d) Explain ripple counter (2 bit) with logic diagram & timing diagram using JK FF. 7

Q. 5. (a) Difference between RAM & ROM. 2

(b) Discuss the successive approximation method for A/D conversion. 7

(c) Implement the following Boolean function using PLA. 7

$$f_1(A, B, C) = \sum (0, 1, 3, 4)$$

$$f_2(A, B, C) = \sum (1, 2, 3, 4, 5)$$

(d) Explain ROM & draw 8x4 diode matrix ROM with the help of decoder (3x8). 7