

Printed Pages – 4

Roll No. : .....

**322352(28)**

**B. E. (Third Semester) Examination, Nov.-Dec. 2021**

**(New Scheme)**

**(CSE Branch)**

**BASIC ELECTRONICS**

***Time Allowed : Three hours***

***Maximum Marks : 80***

***Minimum Pass Marks : 28***

***Note : Attempt all questions. Part (a) of each question is compulsory. Solve any two parts from (b), (c) and (d) of each question.***

**Unit-I**

1. (a) Define law of junction. 2
- (b) What is diode capacitance? Derive the expression for transition capacitance. 7
- (c) With the help of diagram explain the V-I characteristics of a P-N junction diode. 7

**322352(28)**

**PTO**

[ 2 ]

- (d) For any step-graded junction, prove that 7

$$V_0 = V_T \ln \left( \frac{N_A N_D}{n_i^2} \right)$$

**Unit-II**

2. (a) Explain the necessity of filter at the output of the rectifier. 2
- (b) Draw and explain bridge-rectifier circuit with waveforms. 7
- (c) With the help of neat circuit diagram, explain the working of Zener diode as voltage regulator. 7
- (d) Describe the operation of  $\pi$  filters and calculate its ripple factor. 7

**Unit-III**

3. (a) Define  $\alpha$  and  $\beta$  of transistor. 2
- (b) With neat circuit diagram explain the various current components in a p-n-p transistor. 7


322352(28)

[ 3 ]

- (c) Explain the input and output characteristics of a transistor in CB configuration. 7
- (d) Explain what is the 'Early Effect', and state its consequences. 7

**Unit-IV**

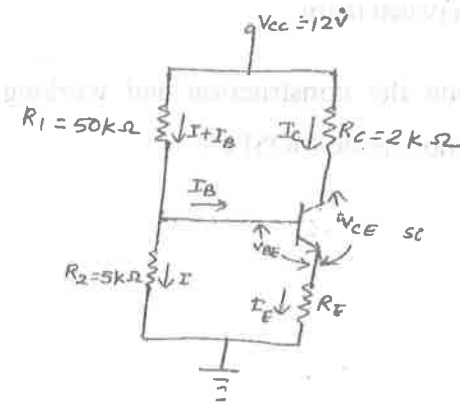4. (a) Define three stability factors. 2
- (b) For collector to base bias circuit, determine  $s'$  and  $s''$ . 7
- (c) For the circuit shown in fig1,  $I_c = 2\text{mA}$ ,  $\beta = 100$ , calculate.  $R_E$ ,  $V_{CE}$  and stability factors. 7



322352(28)

PTO

[ 4 ]

(d) Explain the diode compensation technique. 7

### Unit-V

5. (a) Draw and explain small signal model of FET at low frequency. 2

(b) Sketch the drain characteristics of a JFET and explain it before and after pinch off. 7

(c) Define JFET parameters : 7

(i) Transconductance ( $g_m$ )

(ii) Drain resistance ( $r_d$ )

(iii) Amplification factor ( $\mu$ ) and give relation between them.

(d) Explain the construction and working of the depletion mode MOSFET. 7