

Printed Pages – 7

Roll No. :

328314(28)

B. E. (Third Semester) Examination, April-May 2021

(Old Scheme)

(AEI, CSE, EI, ET&T & IT Engg. Branch)

NETWORK ANALYSIS and SYNTHESIS

Time Allowed : Three hours

Maximum Marks : 80

Minimum Pass Marks : 28

Note : Part (a) of every question is compulsory of 2 marks each. Attempt any two from part (b), (c) and (d) of 7 marks each.

1. (a) Define initial and final value theorem. Solve the below problem :

$$F(s) = \frac{5s+3}{s(s+1)} \text{ for initial value.}$$

2

- (b) In the circuit shown, the switch K is opened at $t = 0$. At $t = 0+$, calculate v , dv/dt and d^2v/dt^2 .

[2]

If $I = 10 \text{ A}$, $R = 1000 \Omega$, $C = 1 \mu\text{F}$.

7

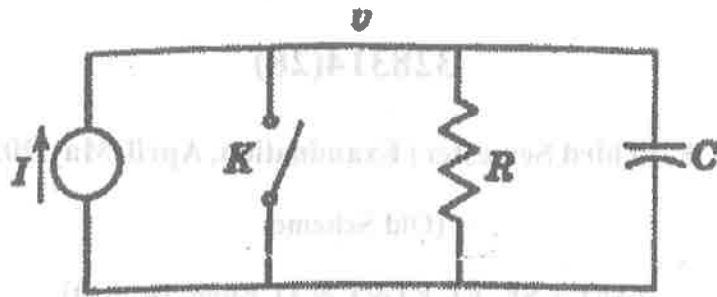


Fig. (1)

(c) At $t = 0$, a switch is closed, connecting a voltage source $V = V \sin \omega t$ to a series RL circuit given below. By the method of Laplace transformation, show that the current is given by the following equation :

7

$$i(t) = \frac{V}{Z} \sin(\omega t - \phi) + \frac{\omega L V}{Z^2} e^{-Rt/L}$$

where $Z = \sqrt{R^2 + (\omega L)^2}$ and $\phi = \tan^{-1} \frac{\omega L}{R}$

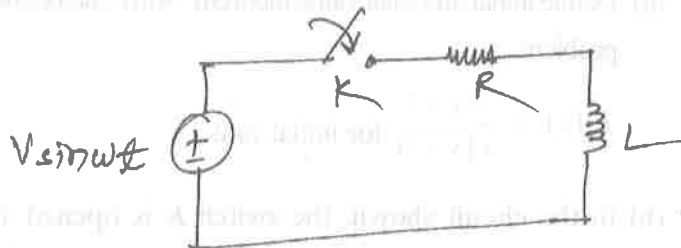


Fig. (2)

[3]

(d) In the network shown, the voltage source follows the law $v(t) = ve^{-\alpha t}$, where v is a constant. The switch is closed at $t = 0$,

7

- (i) Solve for the current assuming that $\alpha = R/L$
- (ii) Solve for the current assuming that $\alpha \neq R/L$

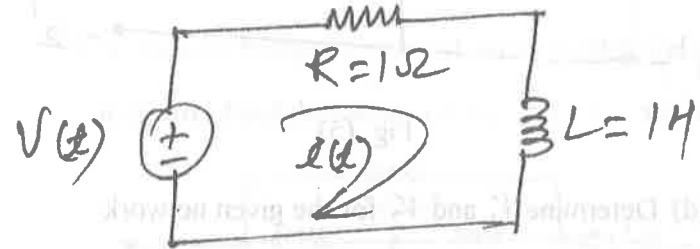


Fig. (3)

- 2. (a) Write down the formula for conversion of z parameters in terms of h parameter. 2
- (b) Find out the Y and Z parameters for the given network : 7

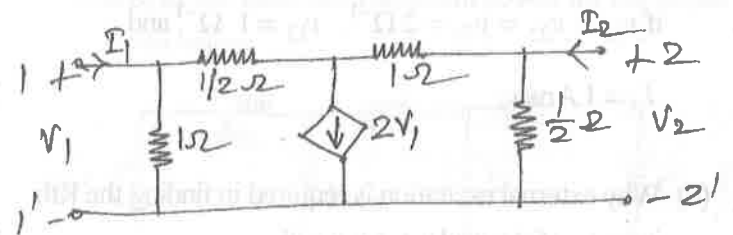


Fig. (4)

[4]

(c) For the figure shown find the value of h parameter : 7

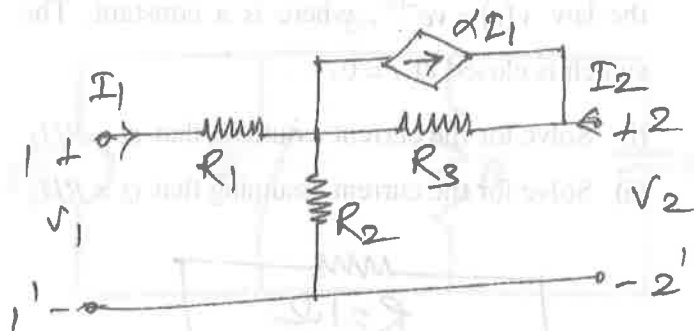


Fig. (5)

(d) Determine V_1 and V_2 for the given network

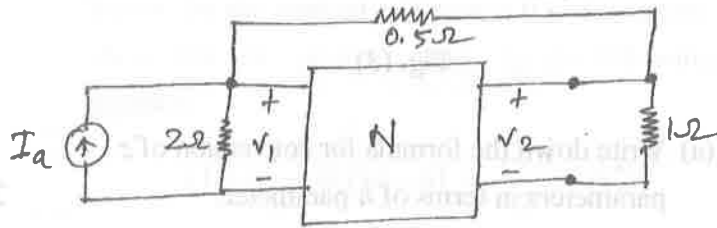


Fig. (6)

if $y_{11} = y_{22} = y_{21} = 2 \Omega^{-1}$, $y_{12} = 1 \Omega^{-1}$ and

$I_a = 1$ Amp.

3. (a) Why external excitation is required in finding the R_{th} in case of dependent sources?

[5]

(b) For the network shown, find out the equivalent Thevenin's network :

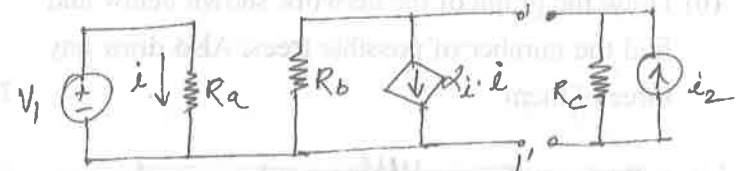


Fig. (7)

(c) A resistive bridged T network (two-port) is shown in figure. Find the values of G_{12} , Z_{12} , Y_{12} and α_{12} .

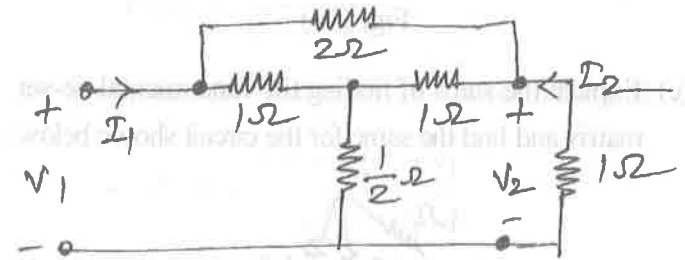


Fig. (8)

(d) Find the value of R_L for maximum power transfer as well as the value of maximum power for the circuit given below.

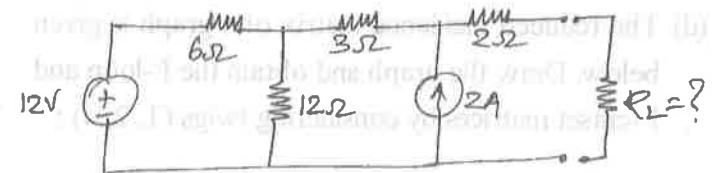


Fig. (9)

[6]

4. (a) Define tree and co-tree. 2
 (b) Draw the graph of the network shown below and find the number of possible trees. Also draw any three of them. 7

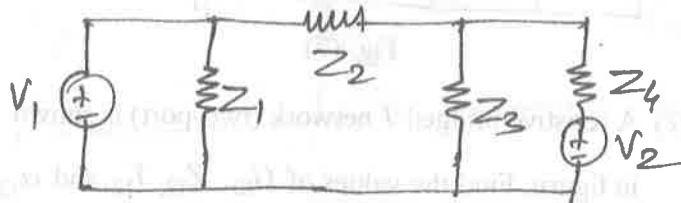


Fig. (10)

- (c) Explain the steps of finding the fundamental tie-set matrix and find the same for the circuit shown below : 7



Fig. (11)

- (d) The reduced incidence matrix of a graph is given below. Draw the graph and obtain the F-loop and F-cutset matrices by considering twigs (1, 2, 4) : 7

[7]

$$A = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \end{matrix} \\ \begin{matrix} a \\ b \\ c \end{matrix} & \begin{bmatrix} 0 & 0 & 1 & 1 & 1 & 0 & -1 \\ 0 & 1 & 0 & 0 & -1 & 1 & 1 \\ -1 & 0 & -1 & 0 & 0 & -1 & 0 \end{bmatrix} \end{matrix}$$

5. (a) What are the conditions for a function to be P. R. F.? 2
 (b) Test whether the following polynomial is Hurwitz or not? Find the condition if any. 7

$$F(s) = \frac{s+a}{s^2+bs+c}$$

- (c) Synthesize the network in Foster form I and II. 7

$$Z(s) = \frac{(s^2+1)(s^2+9)}{s(s^2+4)}$$

- (d) Synthesize the network in Cauer form I and II. 7

$$Z(s) = \frac{s^4+10s^2+9}{s^2+4s}$$