

Printed Pages – 9

Roll No.

328354(28)

B. E. (Third Semester) Examination, April-May 2021

(New Scheme)

(Et & T Branch)

NETWORK ANALYSIS & SYNTHESIS

Time Allowed : Three hours

Maximum Marks : 80

Minimum Pass Marks : 28

Note : Part (a) of every question is compulsory and carries 2 marks. Attempt any two from (b), (c) & (d) and carry 7 marks.

Unit-I

1. (a) Give the equations of h parameter.

2

[2]

- (b) Find out the cut set and tie set matrices for the given graph.

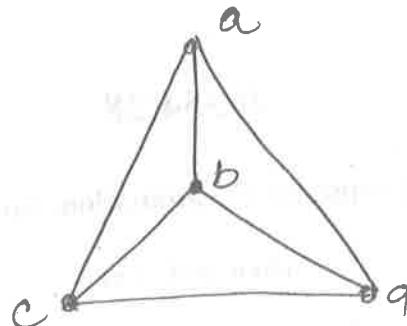


Fig. 1 (b)

- (c) Find out the y and z parameters for given electrical network.

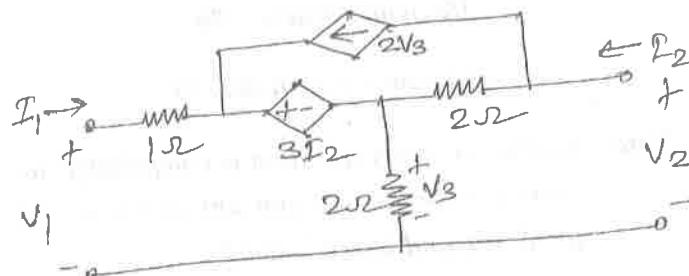


Fig. 1 (c)

- (d) For the given network, determine the value of V_1 and V_2 .

7

[3]

If

$$Y_{11} = Y_{22} = 2 \Omega^{-1}$$

$$Y_{21} = 2 \Omega^{-1}, \quad Y_{12} = 1 \Omega^{-1}$$

and the current source $I_a = 1$ Amp.

7

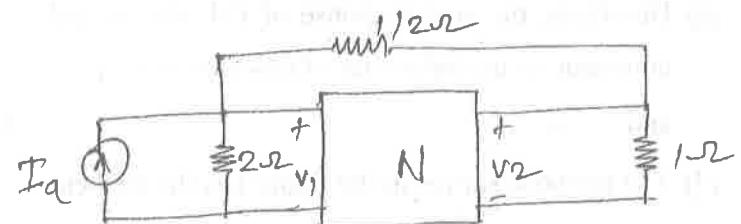


Fig. 1 (d)

Unit-II

2. (a) How does inductor and capacitor behave at $t = 0$ and $t = \infty$.

2

- (b) The network shown below is in the steady state with the switch K closed. At $t = 0$ the switch is opened. Determine the voltage across the switch

$$V_K \text{ and } \frac{dV_k}{dt} \text{ at } t = 0^+.$$

7

[4]

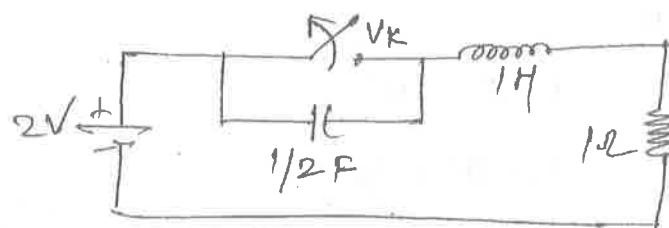


Fig. 2 (b)

- (c) Determine the step response of R-L circuit and comment on the behaviour of inductor at $t = 0$ and $t = \infty$.
- (d) The network shown in the figure has the element value as $R = 1000\Omega$, $L = 1\text{ H}$, $C = 0.1\mu\text{F}$ and $V = 100$ volt. The switch K is changed from position a to b at $t = 0$. At $t = 0^+$, determine i , $\frac{di}{dt}$ & $\frac{d^2i}{dt^2}$.

7

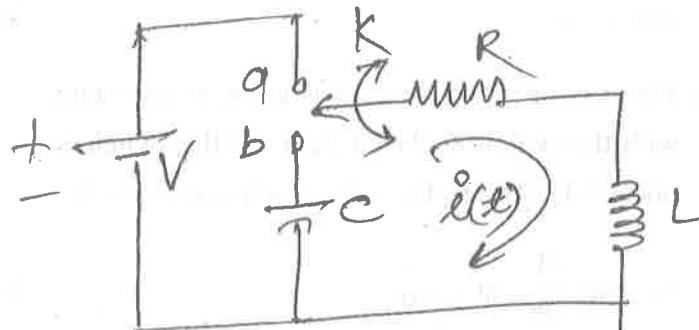


Fig. 2 (d)

328354(28)

[5]

Unit-III

3. (a) What is initial and final value theorem?

2

- (b) Determine the equations of given waveforms.

7

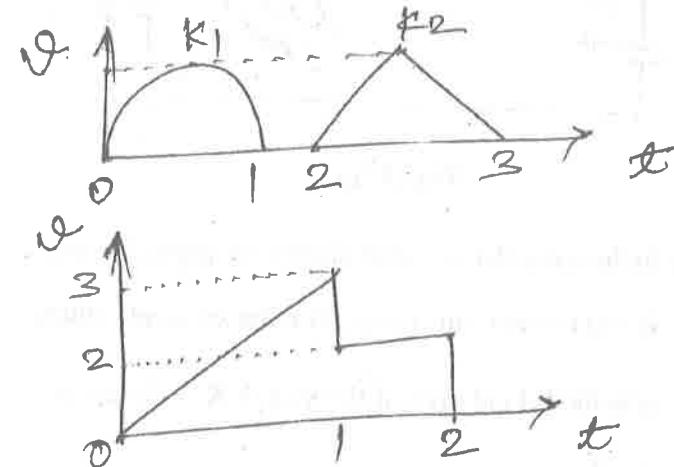


Fig. 3 (b)

- (c) The network of the figure reaches a steady state with the switch K open. At $t = 0$, switch K is closed.

7

Find $i(t)$ for numerical values given, sketch the current waveform and indicate the value of the time constant.

328354(28)

PTO

[6]

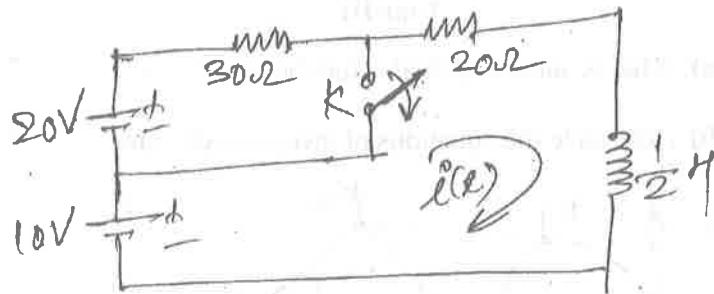


Fig. 3 (c)

- (d) In the series R-L-C circuit shown, the applied voltage is $v(t) = \sin t$ for $t = 0$. For the element values specified. Find $i(t)$, if the switch K is closed at

$$t = 0.$$

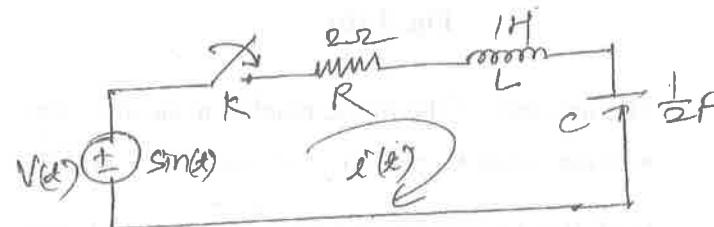


Fig. 3 (d)

Unit-IV

4. (a) Give the condition for maximum power transfer across load.

2

[7]

- (b) For the network shown below, determine the Thevenin's equivalent network for the load R_L .

7

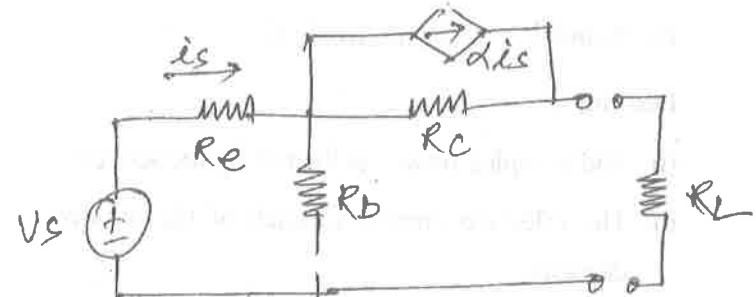


Fig. 4 (b)

- (c) For the given network shown in below figure, show that :

7

$$Y_{12} = \frac{k(s+1)}{(s+2)(s+4)}$$

and determine the value of sign of K .

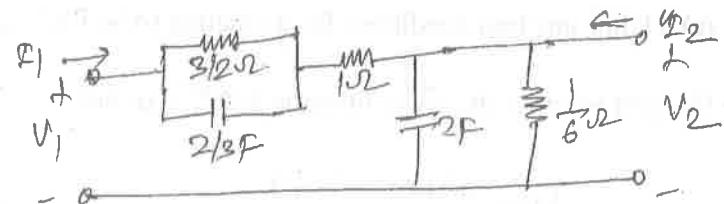


Fig. 4 (c)

[8]

- (d) The network shown in below figure is operated in the sinusoidal steady state , with the element value given and $V = V_0 = 100 \cos^2 t$ V.

7

Determine :

- The complex power delivered by the source
- The effective current in each of the passive elements.

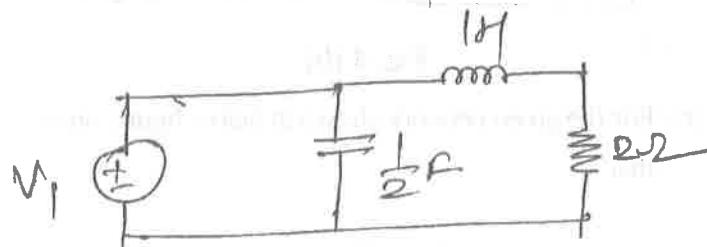


Fig. 4 (d)

Unit-V

5. (a) Define any two conditions for a function to be P.R.F. 2

- (b) Test whether the given function is P.R.F. or not.

$$f(s) = \frac{s^3 + 6s^2 + 7s + 3}{s^2 + 2s + 1}$$

7

- (c) For the given impedance function, obtain forster form I and II.

7

[9]

$$z(s) = \frac{(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

- (d) Find out the cauer form I and II for given impedance function :

7

$$z(s) = \frac{s^4 + 10s^2 + 9}{s^3 + 4s}$$