

**B067313(067)**

**B.Tech. (Third Semester) Examination  
Nov.-Dec. 2020**

**ELECTRONIC DEVICES and DIGITAL CIRCUITS**

***Time Allowed : Three hours***

***Maximum Marks : 100***

***Minimum Pass Marks : 35***

***Note : Attempt all questions. Part (a) is compulsory  
& Attempt any two parts from (b), (c) and  
(d) of each questions.***

**Unit-I**

1. (a) What is static resistance of a diode? 4

(b) Sketch the V-I characteristics of a diode and explain

it. 8

[ 2 ]

- (c) Explain the working of a half wave rectifier with circuit diagram and waveforms. 8
- (d) Explain Zener breakdown and differentiate it from Avalanche breakdown. 8

### Unit-II

2. (a) Why is the base most lightly doped? 4
- (b) Draw the circuit diagram and explain the working of a transistor in CB configuration. 8
- (c) With a neat diagram explain the V-I characteristics of JFET. 8
- (d) Draw and explain the construction and working of a depletion type MOSFET. 8

### Unit-III

3. (a) Define universal gates. 4
- (b) Simplify the following Boolean function by K-map. 8

$$F = \sum m(0, 1, 2, 3, 5, 7, 8, 9, 10, 12)$$

[ 3 ]

- (c) Explain all logic gates in brief. 8
- (d) Explain the basic concept of TTL to implement universal logic gate. 8

### Unit-IV

4. (a) Define Combinational circuit with basic block diagram. 4
- (b) Explain FULL-ADDER using two HALF Adder with its logic diagram. 8
- (c) Define Multiplexer. Explain 2-input and 4-input Multiplexer with suitable block diagram. 8
- (d) Define Decoder. Explain 3 to 8 Line Decoder with Block Diagram. 8

### Unit-V

5. (a) What is Shift Register? 4
- (b) Draw the conversion of JK Flip to RS Flip flop using all necessary steps. 8
- (c) Explain parallel in serial out shift register using block diagram. 8

- (d) Design a D- Flip Flop using 8
- (i) Logic Diagram
  - (ii) Graphical Symbol
  - (iii) Truth Table
  - (iv) Characteristics Table
  - (v) Excitation Table
  - (vi) Characteristics Equation (K-map Table)