

Printed Pages – 6

Roll No. ....

**328453(28)**

**B. E. (Fourth Semester) Examination, 2020**

(New Scheme)

APR-MAY 2022

(ET & T Engg.)

**ANALOG ELECTRONICS**

*Time Allowed : Three hours*

*Maximum Marks : 80*

*Minimum Pass Marks : 28*

*Note : In each question part (a) is compulsory and carry 2 marks. Solve any two parts from (b), (c) & (d) and carry 7 marks. Assume suitable data if required.*


**Unit-I**

1. (a) State Miller's Theorem.
- (b) Find  $h_{fe}$  in terms of the CB h-parameters.
- (c) The transistor amplifier shown below uses a transistor

[ 2 ]

whose h-parameters are given as  $h_{ie} = 1.1 \text{ k}$ ,  $h_{fe} = 50$ ,  $h_{re} = 2.5 \times 10^{-4}$  and  $h_{oe} = 25 \mu \text{ A/V}$ . Calculate

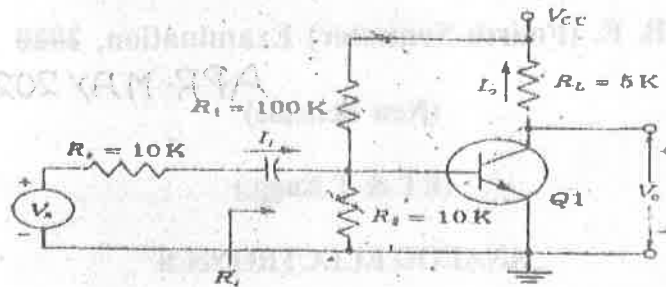$A_i = I_o/I_i$ ,  $A_v$ ,  $A_{vs}$ ,  $R_0$  and  $R_i$ .



- (d) What is Darlington pair? Derive expression for input resistance and current gain for Darlington pair.

### Unit-II


2. (a) Discuss the effect of temperature on the base spreading resistance.
- (b) For hybrid- $\pi$  model derive expression for :
- conductance  $g_{b'e}$
  - feedback conductance  $g_{b'c}$
  - base spreading resistance  $r_{bb'}$

328453(28)

[ 3 ]

- (iv) output conductance  $g_{ce}$  in terms of h-parameters.

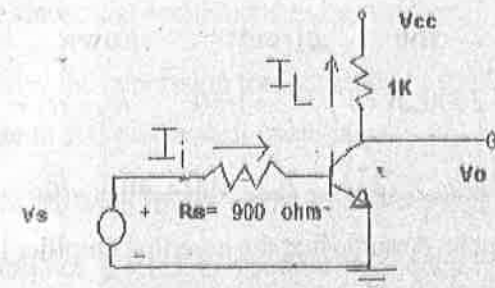- (c) At  $I_c = 1 \text{ mA}$  and  $V_{CE} = 10 \text{ V}$ , a certain transistor data shown  $C_c = 3 \text{ pF}$ ,  $h_{fe} = 200$  and  $\omega_T = 500 \text{ M rad/sec}$ . Calculate  $g_m$ ,  $r_{b'e}$ ,  $C_e$  and  $\omega_\beta$ .
- (d) For hybrid- $\pi$  parameter of transistor used in the circuit shown below are  $g_m = 50 \text{ mA/V}$ ,  $r_{b'e} = 1 \text{ k}\Omega$ ,  $r_{b'c} = 4 \text{ M}\Omega$ ,  $r_{ce} = 80 \text{ k}\Omega$ ,  $C_e = 100 \text{ pF}$  and  $r_{bb'} = 100 \Omega$ . Find (i) Upper 3 dB frequency of current gain  $A_i = I_o/I_i$ , (ii) The value of voltage gain  $A_{vs} = V_o/V_s$  at frequency of part (i).



328453(28)

PTO

## Unit-III

3. (a) Write the types of distortions in an amplifier.
- (b) Obtain an expression for the second harmonic distortion  $D_2$  in terms of  $G_1$ ,  $G_2$  and  $I_{bm}$ . Where  $i_c = G_1 i_b + G_2 i_b^2$  and  $i_b = I_{bm} \cos \omega t$ .
- (c) How push-pull arrangement of an amplifier reduces harmonic distortion? Explain by drawing a ckt of class A push pull amplifier.
- (d) Define rise time of an amplifier, and how it is related with upper 3-dB frequency of the amplifier?


## Unit-IV

4. (a) What are the affects of topology on input and output resistance?
- (b) Derive the expression for input and output resistances in case of voltage shunt topology.
- (c) For the circuit shown below,  
 $A = -2000$ ,  $\beta = V_f/V_o = 1/50$ ,  $R_s = R_E = R_C = R_L = 3k\Omega$ ,  $h_{ie} = 2k\Omega$ ,  $h_{ie} = 200$  and  $h_{re}$ ,  $h_{oe}$  are negligible. Assume that the inverting amplifier input

resistance is infinite and that the feedback network can be represented by an ideal controlled voltage source.

Find (i)  $V_i$  as function of  $V_s$  and  $V_f$  (ii)

$$A_{vf} = V_o/V_s = A V_i/V_s.$$

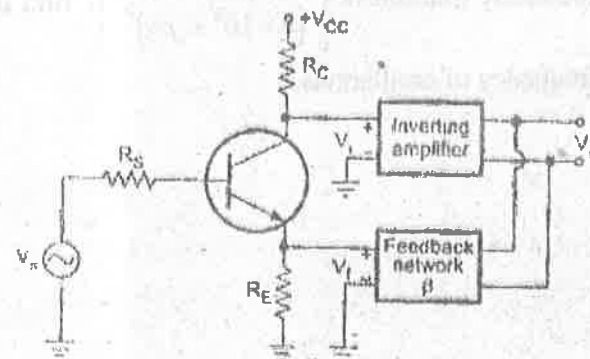

- (d) Explain the effect of feedback on amplifier bandwidth and stability?

## Unit-V

5. (a) Give the two Barkhausen conditions required in order for sinusoidal oscillations to be sustained?
- (b) Derive the expression for frequency of oscillation in case of RC phase shift oscillator?
- (c) What is Wein Bridge oscillator? Show that for such oscillator  $\beta = 1/3$  at resonant frequency.

[ 6 ]

(d) The gain of a forward amplifier is frequency

dependent and given by  $A = \left[ \frac{-1 \times 10^7}{j\omega} \right]$ . If the

feedback fraction is  $\left[ \frac{9 \times 10^3}{(6 \times 10^3 + j\omega)^2} \right]$ , find the

frequency of oscillations.