

B028412(028)

**B. Tech. (Fourth Semester) Examination,
April-May 2022**

(AICTE Scheme)

(Electronics & Telecommunication Engineering Branch)

ANALOG CIRCUITS

Time Allowed : Three hours

Maximum Marks : 100

Minimum Pass Marks : 35

Note : All questions are compulsory. Part (a) of each question is compulsory and carries 4 marks. Attempt any two parts from (b), (c) and (d) from each question which carry 8 marks each. Assume suitable data whenever required.


Unit-I

1. (a) State Miller's theorem and Dual of Miller's theorem.

[2]

(b) For the amplifier shown compute $A_I = \frac{I_0}{I_i}$, A_v , A_{vs}

and R_i .

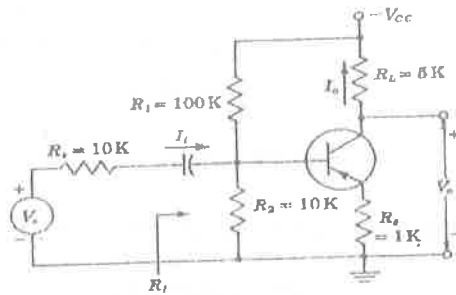


(c) (i) Show that the exact expression for h_{fb} in terms of CE hybrid parameters is :

$$h_{fb} = - \frac{h_{fe}(1 - h_{re}) + h_{ie}h_{oe}}{(1 + h_{fe})(1 - h_{re}) + h_{ie}h_{oe}}$$

(ii) The cascade configuration shown is the tandem emitter follower. Find the input resistance R_i if $h_{ie} = h_{re} = h_{oe} = 0$ and h_{fe} is the same for each transistors Q_1 to Q_N .

[3]

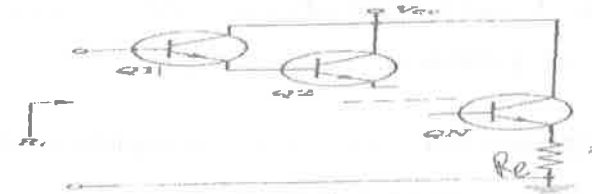

(d) Draw h-parameter equivalent circuit for a generalized transistorized amplifier and derive expressions for A_i , A_v , R_i .

Unit-II

2. (a) What is the meaning of upper 3-dB frequency and lower 3dB frequency? Show it on frequency response.

(b) (i) Define Transconductance g_m and derive the expression for it.

(ii) Also prove that : $g_{ce} = h_{oe} - h_{fe} \cdot g_{b'c}$

(c) The following low frequency parameters are known for a given transistor at $I_C = 1.3 \text{ mA}$, $V_{CE} = 10 \text{ V}$ at room temperature and h-parameters are $h_{fe} = 50$, $h_{je} = 1100 \text{ } \Omega$, $h_{re} = 2.5 \times 10^{-4}$, $h_{oe} = 24 \text{ } \mu\text{A/V}$. At the same point $F_T = 50 \text{ MHz}$, $CC =$

[4]

3pF. Compute all the values of hybrid π parameter of a CE transistor.

- (d) Analyse common emitter transistor amplifier at high frequencies for short circuit current gain. Also prove that $F_T = h_{fe} \cdot F_\beta$.

Unit-III

3. (a) Define the following types of distortion :
- Non-Linear Distortion
 - Frequency Distortion
- (b) Explain the step response of an amplifier. Derive the expression for rise time and sag. Briefly why this happens?
- (c) Explain the effect of cascading on Bandwidth with the help of expression for higher and lower cut-off frequencies.
- (d) It is desired that the voltage gain of a RC coupled amplifier at 60 Hz should not decrease by more than 10% from its midband value. Show that the coupling capacitance C must be at least equal to

B028412(028)

[5]

$5.5/R'$ where $R' = R_o' + R_i'$ is expressed in $k\Omega$ and C in microfarad.


Unit-IV

4. (a) Draw a feedback amplifier in one-line block diagram form. What is the relation between transfer gain with feedback A_f and that without feedback A for a negative feedback amplifier.

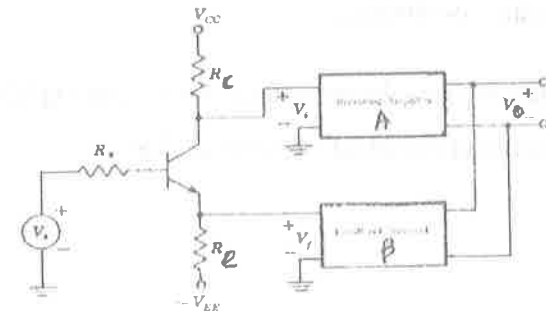- (b) For the circuit shown find the ac voltage V_i as a function of V_s and V_f . Assume that the inverting amplifier input resistance is infinite and that $A = A_v = -1000$.

$$\beta = V_f/V_o = 1, R_e = R_c = R_c = 1K,$$

$$h_{ie} = 1K, h_{re} = h_{oe} = 0, h_{fe} = 100. \text{ Find } A_{vf} = V_o/V_s.$$



B028412(028)

PTO

[6]

- (c) What is the effect of negative feedback on input impedance of voltage shunt and current shunt amplifier?
- (d) Enumerate the effects of negative Feedback on the various characteristics of the amplifier.

Unit-V

5. (a) Give the two Barkhausen conditions required in order for sinusoidal oscillations to be sustained.
- (b) Draw the circuit and explain the working of Hartley oscillator using BJT. Write expression for frequency of oscillation.
- (c) What is Weign bridge oscillator? Show that for such an oscillator gain of amplifier should be $A > 3$ to produce oscillations.
- (d) What is piezoelectric effect? Draw and explain ac equivalent circuit of a crystal oscillator.