

Printed Pages – 4

Roll No. : .....

**328833(28)**

APR-MAY 2022

**B. E. (Eighth Semester) Examination, 2020**

**(New Scheme)**

**(ET & T Engg. Branch)**

**POWER ELECTRONICS**

***Time Allowed : Three hours***

***Maximum Marks : 80***

***Minimum Pass Marks : 28***

***Note : Attempt all questions. Part (a) <sup>of</sup> is each question is compulsory. Attempt any two parts from (b), (c) and (d).***

**Unit-I**

**1. (a) Write the light Triggering methods for Thyristor**

**TURN-ON.**

**2**

**328833(28)**

**PTO**

[ 2 ]

- (b) Sketch the two Transistor Analogy of SCR with expression and explain it. 7
- (c) Describe the different modes of operation of a SCR with the help of its VI characteristics. 7
- (d) Write detail notes on : (any one) 7
- (i) IGBT
  - (ii) Power MOSFET
  - (iii) SBS/GTO

### Unit-II

2. (a) Why commutation circuit is required for SCR? 2
- (b) What are the problem associated with series connection of SCR's. Derive an expression for optimum value of Resistance of static equalizing circuit. 7
- (c) Explain the Half wave converter with RLE loads by using suitable waveform. 7
- (d) A relaxation oscillator using an UJT, is to be designed for triggering an SCR.

[ 3 ]

The UJT has the following data :

- (I)  $\eta = 0.72$ ,  $I_p = 0.6$  mA,  $V_p = 18$  V,  $V_u = 1.0$  V,  
 $I_v = 2.5$  mA,  $R_{BB} = 5$  k $\Omega$ , Normal leakage current with emitter open = 4.2 mA.

- (II) The firing freq = 2 kHz;  $c = 0.04$   $\mu$ F

Calculate :

- (i)  $R_1$  (ii)  $R_2$  and (iii)  $R_2$ .

### Unit-III

3. (a) What is Inversion mode of converter? 2
- (b) Compare the Symmetrical and Asymmetrical circuit of bridge converter (single phase). 7
- (c) Draw the full wave three-phase bridge converter and explain with suitable waveform. 7
- (d) What is 1  $\phi$  dual converter? Explain its working with waveform. 7

### Unit-IV

4. (a) Write the Chopper Control Technique. 2

- (b) Explain Mc-Murrey full bridge inverter with suitable circuit diagram and waveform. 7
- (c) Write short note on : (any one) 7
- (i) Buck-Boost chopper
- (ii) Jones chopper
- (d) A step-up chopper has input voltage of 220 V and output voltage of 660 V. If the conducting time of thyristor-chopper is 100  $\mu$  s. (i) Compute the pulse width of output voltage. (ii) In case O/P voltage pulse width is halved for constant frequency operation, find the average value of new O/P voltage. 7

### Unit-V

5. (a) Write application of cycloconverter. 2
- (b) Draw and explain of single phase AC voltage controller with RL load. 7
- (c) Explain the principle of Integral cycle control with their voltage expression. 7
- (d) Describe the basic principle of working of single-phase to single-phase step-down cycloconverter. 7