

Printed Pages – 4

Roll No. : .....

**333353(33)**

**B. E. (Third Semester) Examination, Nov.-Dec. 2021**

**(New Scheme)**

**(IT Engg. Branch)**

**BASIC ELECTRONICS & NETWORK THEORY**

*Time Allowed : Three hours*

*Maximum Marks : 80*

*Minimum Pass Marks : 28*

*Note : Part (a) is compulsory and of 2 marks. Attempt any two parts from (b), (c) & (d) carry 7 marks each.*

**Unit-I**

1. (a) Define KVL & KCL for writing Network.


(b) Explain maximum power transfer theorem with example.

**333353(33)**

**PTO**

[ 2 ]

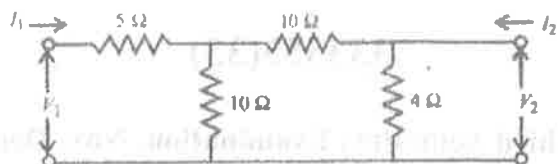- (c) Example Thevenin's theorem with example.
- (d) Find Z parameter for the network shown below.



### Unit-II

2. (a) What do you mean by rectifier?
- (b) Draw the ckt diagram of full wave rectifier and explain its working with waveform. Find expression for efficiency.
- (c) How many capacitances are in effective in diode? Explain them with characteristics and derivation.
- (d) Write and prove Diode equation.

$$I = I_0 (e^{V/V_T} - 1)$$

### Unit-III

3. (a) Explain about doping concentration of different

[ 3 ]

region of transistor.

- (b) Write different current components of p-n-p Transistor with diagram.
- (c) Draw and explain the all characteristics of common base configuration of transistor.
- (d) Explain early effect with diagram.

### Unit-IV

4. (a) Explain the reason for keeping operating point of transistor fixed.
- (b) What is bias compensation? Give compensation for  $V_{be}$ .
- (c) Explain the operation of collector to base bias ckt. and find stability factor.
- (d) Write short notes on :
- (i) Stability factor
  - (ii) Selection of operating point

### Unit-V

[ 4 ]

5. (a) What do you mean by FET?
- (b) With structure, explain the characteristics of JFET.
- (c) Comparison between JFET and MOSFET.
- (d) Write n-channel depletion type MOSFET with neat diagram and explain its characteristics.