

B033413(033)

B. Tech. (Fourth Semester) Examination

April-May 2022

(AICTE Scheme)

(IT Branch)

ANALOG ELECTRONIC CIRCUITS

Time Allowed : Three hours

Maximum Marks : 100

Minimum Pass Marks : 35

***Note : Part (a) is compulsory from each unit.
Attempt any two parts from (b), (c) and (d)
to each unit. Part (a) is of 4 marks and part
(b), (c) and (d) has 8 marks.***

Unit-I

1. (a) Write diode current equation and explain each term.
(b) Show that I_0 increases by 11% per degree rise temperature for Germanium.

[2]

- (c) Derive the expression for DC current, RMS current, DC power, AC power, Efficiency, Ripple factor for Half Wave Rectifier.
- (d) Write the short note on Zener Breakdown and Avalanche Breakdown.

Unit-II

2. (a) Why an ordinary junction transistor is called bipolar?
- (b) Draw and explain the characteristics of common-emitter configuration of transistor.
- (c) Explain early effect in transistor with suitable diagram.
- (d) Draw and explain the Ebers-Moll model of a transistor.


Unit-III

3. (a) What is the requirement of h-parameter models?
- (b) Derive the expression for CE short circuit current gain A_i as a function of frequency.
- (c) Derive an expression for A_p , R_i , A_v and R_o using exact analysis.

B033413(033)

[3]

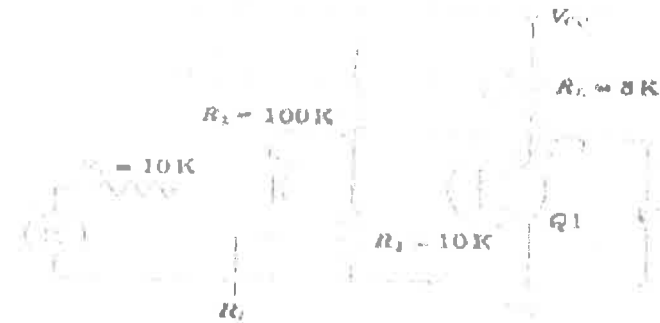- (d) For the circuit shown, calculate $A_i = I_o/I_p$, A_v , A_{vsw} , R_i and R_o . Transistor h parameter are as follows $h_{jc} = 1.1 \text{ K}$, $h_{re} = 2.5 \times 10^{-4}$, $h_{fe} = 50$, $h_{oc} = 25 \mu \text{ A/V}$.



Unit-IV

4. (a) What do you mean by Fidelity of an amplifier?
- (b) Draw the two stage RC coupled amplifiers and explain its response in LF and HF.
- (c) Explain Noise Figure and show the procedure for measurement of noise figure.
- (d) Explain magnitude bode plot of a 2-pole transfer function.

Unit-V

B033413(033)

PTO

[4]

5. (a) Differential between positive and negative feedback.
- (b) Explain Barkhausen Criterion and condition of oscillation.
- (c) Discuss feedback amplifier topologies.
- (d) Draw a circuit crystal controlled oscillator. Explain its working principle in details.