

Printed Pages – 4

Roll No. :

B024314(024)

**B. Tech. (Third Semester) Examination,
Nov.-Dec. 2021**

A) CTE (New Scheme)

DIGITAL ELECTRONICS

Time Allowed : Three hours

Maximum Marks : 100

Minimum Pass Marks : 35

Note : Attempt all questions. Part (a) of each question is compulsory. Attempt any two parts from (b), (c) and (d) of each question.

Unit-I

1. (a) What is Parity bit? Explain. 4

(b) (i) Convert gray code 101011 into its binary equivalent. 2

B024314(024)

PTO

[2]

- (ii) Convert $(85.63)_{10}$ to binary. 2
- (iii) Convert $(2AC5.D)_{16}$ to decimal. 2
- (iv) Convert $(475.25)_8$ to decimal. 2
- (c) What is the simplified form of the Boolean expression?
- (i) $ABC' + ABC + A'BC + A'BC'$ 2
- (ii) $(A' + B)(A + B)$ 2
- (iii) $X = B + A \cdot B' + A \cdot B$ 2
- (iv) $(125)_R = (203)_S$, find out the value of radix R. 2
- (d) The message below has been coded in the even parity humming code transmitted through a noise channel. Code the message assuming that it must have a single error occurred in each word code.
(0111001) 8

Unit-II

2. (a) Distinguish between sum-of-products and product-of-sums. 4

B024314(024)

[3]

- (b) Implement the following function with a Multiplexer. 8

$$F(A, B, C, D) = \sum(0, 1, 3, 4, 8, 9, 15)$$

- (c) Simplify the expression given below using K map. 8

$$Y = \sum m(0, 1, 5, 9, 13, 14, 15) + d(3, 4, 7, 10, 11)$$

- (d) Determine the prime - implicants of the function. 8

$$F(W, X, Y, Z) = \sum(1, 4, 6, 7, 8, 9, 10, 11, 15)$$

Unit-III

3. (a) What is basic function flip-flop? 4
- (b) Convert T FLIP-FLOP to D FLIP-FLOP. 8
- (c) Explain JK flip-flop with suitable logic diagram, & explain its operation. 8
- (d) Explain right counter & also explain synchronous counters. 8

Unit-IV

4. (a) Explain digital to analog converter. With suitable example. 4

B024314(024)

PTO

[4]

- (b) Explain weighted resistor/converter. 8
- (c) Describe A/D converter with example. 8
- (d) Explain R-2R Ladder D/A converter. 8

Unit-V

- 5. (a) Explain memory organization. 4
- (b) What is programmable logic array? How it differs from ROM? 8
- (c) Explain classification and characteristics of memories with example. 8
- (d) Explain ROM & also explain types of ROM. 8

Printed Pages – 6

Roll No. :

B028312(028)

B. Tech. (Third Semester) Examination,

Nov.-Dec. 2021

(AICTE Scheme)

(Electronics & Telecommunication Engineering Branch)

ELECTRONICS DEVICES

Time Allowed : Three hours

Maximum Marks : 100

Minimum Pass Marks : 35

Note : All questions are compulsory. Part (a) of each question is compulsory and attempt any two parts from parts (b), (c) and (d). Part (a) is of 4 marks and part (b), (c) and (d) each are of 8 marks. Assume suitable data whenever required.

Unit-I

1. (a) A potential difference of 10 V is applied longitudinally to a rectangular specimen of intrinsic germanium of length 25 mm, width 4 mm and thickness 1.5 mm. Find the total current if intrinsic carrier concentration

B028312(028)

PTO

[2]

is $2.5 \times 10^{19} / \text{m}^3$, $\mu_e = 0.38 \text{ m}^2 \text{ V}^{-1} \text{ s}^{-1}$, $\mu_h = 0.18 \text{ m}^2 \text{ V}^{-1} \text{ s}^{-1}$.

- (b) Draw the energy band diagram of an open circuited p-n junction. Indicate Fermi level and contact potential E_0 ?
- (c) In intrinsic GaAs, the electron and hole mobilities are 0.85 and $0.04 \text{ m}^2/\text{V-s}$ respectively and corresponding effective masses are $0.068 m_0$ and $0.5 m_0$ respectively where m_0 is the rest mass of an electron. If the energy gap of GaAs at 300 K is 1.43 eV , calculate the intrinsic carries concentration and conductivity.
- (d) Derive the following expression for a step graded

$$\text{junction } V_0 = V_T \log_e \left(\frac{N_A N_D}{n_i^2} \right).$$


Unit-II

2. (a) (i) Define ripple factor and transformer utilization factor.

B028312(028)

[3]

 - (ii) Why π -filters are not suitable for varying loads?
- (b) Describe bridge rectifier. How does it differ from full wave rectifier using two diodes only? What do you understand by PIV?
- (c) Explain the working of zener diode as a voltage regulator?
- (d) For the network shown in below figure, determine the range of RL and IL that will result in VRL being maintained at 10 V , also determine the maximum wattage rating of diode.



Unit-III

3. (a) Explain following terms :
- (i) Operating Point

B028312(028)

PTO

[4]

- (ii) Punch through
 - (iii) Thermal Runaway
 - (iv) Advantage of CE over CB and CC
- (b) (i) Draw and explain the current components in a pnp transistor?
- (ii) For a certain npn transistor $I_C = 5 \text{ mA}$, $I_B = 50 \mu\text{A}$ and $I_{CBO} = 1 \mu\text{A}$. Calculate α , β and I_E . Determine the new level of I_B required to make $I_C = 10 \text{ mA}$.
- (c) Explain Early effect. Also explain qualitatively the three consequences of Base width modulation?
- (d) List various Bias Compensation Technique and explain any two in brief.

Unit-IV

4. (a) (i) Why FET is called a voltage controlled device?
- (ii) Explain why does the drain current I_D not reduced to zero even after the channel is pinched off?

B028312(028)

[5]

- (b) Explain drain characteristics of n-channel JFET. Explain shape of characteristics and identify regions.
- (c) (i) Compare JFET with BJT.
- (ii) Why input impedance of FET is high?
- (iii) Obtain the expression for the Pinch OFF voltage V_P in case of n-channel JFET?
- (d) An n-channel JFET has $I_{DSS} = 10 \text{ mA}$ and pinch off voltage $V_P = -4 \text{ V}$. Find the drain current for $V_{GS} = -2 \text{ V}$. If transconductance g_m of a JFET with the same I_{DSS} at $V_{GS} = 0 \text{ V}$ is 4 m Mho, find the pinch off voltage.

Unit-V


5. (a) Explain working of MOSFET as a switch.
- (b) (i) Which MOSFET is called as Normally ON MOSFET and NORMALLY OFF MOSFET and why?
- (ii) Make comparison between JFET and MOSFET.
- (c) Define Pinch OFF voltage, threshold voltage and draw drain characteristics and transfer characteristics for n-channel E MOSFET.

B028312(028)

PTO

[6]

 (d) Determine I_{DQ} and V_{DSQ} for Enhancement type MOSFET for given circuit.



Printed Pages – 4

Roll No. :

B028313(028)

**B. Tech. (Third Semester) Examination,
Nov.-Dec. 2021**

(AICTE Scheme)

(Electronics & Telecommunication Engg. Branch)

DIGITAL SYSTEM DESIGN

Time Allowed : Three hours

Maximum Marks : 100

Minimum Pass Marks : 35

***Note : Part (a) of all the questions is compulsory.
Part (a) carries 4 marks. Attempt any two from
from part (b), (c) and (d). Part (b), (c) and (d)
carries 8 marks each.***

Unit-I

1. (a) Perform the following BCD addition :

84

[2]

(i) $26 + 13$

(ii) $579.6 + 636.8$

(b) Prove the following Boolean expression : 8

(i) $A + A'B = A + B$

(ii) $AB + A'C + BC = AB + A'C$

(c) Reduce the expression

$$f = \sum m(1, 5, 6, 12, 13, 14) + d(2, 4)$$

and implement the real minimal expression using universal logic. 8

(d) Realize the XOR function using :

(i) AOI Logic,

(ii) NAND Logic, and

(iii) NOR Logic 8

Unit-II

2. (a) Design Full Adder using two Half Adders. 4

(b) Design a 4-line-to-16-line Decoder using 3-line-to-8-line Decoder. 8

B028313(028)

[3]

(c) Implement the following logic function using an 8XI MUX

$$F(A, B, C, D) = AB' + BD + B'CD' \quad 8$$

(d) Design 4-bit BCD Adder and draw its logic diagram. 8

Unit-III

3. (a) What is meant by race around condition in flip flops and how this problem can be eliminated? 4

(b) Convert J-K flip flop to S-R Flip flow. 8

(c) Design a 4-bit universal shift register and draw the logic circuit diagram. 8

(d) Design a Synchronous BCD Counter using J-K Flip flops. 8

Unit-IV

4. (a) Define Mealy model and Moore model. 4

(b) What is a serial adder? Explain its working with the help of a state diagram and a state table. 8

(c) Draw and explain the ASM chart for sequence detector. 8

B028313(028)

PTO

[4]

- (d) Design 3-bit odd parity generator with the help of a state diagram and a state table. 8

Unit-V

5. (a) Compare the logic families in terms of commonly used specification parameters. 4
- (b) With the help of a neat diagram, explain the working of IIL NAND and NOR Gates. 8
- (c) With the help of a neat diagram, explain the working of a two-input TTL NAND gate with Totem-pole output. 8
- (d) With the help of a neat diagram, explain the working of a two-input ECL OR/NOR gate. 8

Printed Pages – 8

Roll No.

B028314(028)

**B. Tech. (Third Semester) Examination,
Nov.-Dec. 2021**

(AICTE Scheme)

(Electronics and Telecommunicaton Engg. Branch)

NETWORK THEORY

Time Allowed : Three hours

Maximum Marks : 100

Minimum Pass Marks : 40


Note : Attempt all questions. Part (a) of each question is compulsory and carries 4 marks. Solve any two parts from part (b), (c) & (d) and carries 8 marks each.

Unit-I


1. (a) Write down the condition for maximum power transfer.

[2]

 - (b) Find out the Thevenin's equivalent circuit for the given network :



 - (c) The network shown in below figure is operated in the sinusoidal steady state, with the element values given and $V = 100 \cos 2t$. Determine :
- The complex power delivered by the source.
 - The effective current in each of the passive elements.




B028314(028)

[3]

 - (d) For the given network shown that :


$$V_{\theta} = \frac{V_1}{2} [1 + a - ab] \text{ and } z_{\theta} = \frac{3-b}{2}$$

where V_{θ} = Thevenin's volt, z_{θ} = Thevenin's resistance.



Unit-II

 - What is the behaviour of inductor and capacitor under transient and steady state condition?
 - Derive and explain the step response of RC circuit.
 - The network of the figure reaches a steady state with the switch K open. At $t = 0$ the switch K is closed. Find $i(t)$ for numerical values given and sketch the current waveform. Also indicate the value of time constant.




B028314(028)

PTO

[4]

 - (d) K is opened at $t = 0$, solve for V , dv/dt and d^2v/dt^2 at $0+$, If $I = 1 \text{ A}$, $R = 100 \Omega$, $L = 1 \text{ H}$.



Unit-III



3. (a) Define initial and final value theorem.
 (b) In the series RLC circuit shown, the applied voltage is $V(t) = \sin t$ for $t > 0$. For the elements values specified, find $i(t)$. The switch is closed at $t = 0$.



- (c) Synthesize the following waveforms and find out the Laplace transform.

B028314(028)

[5]

  

- (d) State and prove Convolution Theorem. How does it useful for analysis of electrical network?


Unit-IV

4. (a) Give the equations of h parameter.
 (b) The figure shown contains both a dependent current and dependent voltage source. For the element values given, determine the Y and Z parameters :


B028314(028)

PTO


[6]

 

 (c) The network shown below consists of a resistive T and a resistive Π network in parallel. For the element values given, determine Y parameters :



 (d) Determine Z and Y parameter for the given circuit :




Unit-V

5. (a) What is a Sinusoid?

[7]

(b) Explain the basic principle behind sinusoidal steady state analysis. Also give the steps to be followed to find the steady state value of $i(t)$ in R-L circuit for a given excitation of $V = V \cos \omega t$, where V is the real time constant.

(c) For the given network find current.

 

Find : $I(t) = ?$

Given : $R = 1/3 \Omega$

$L = 1/4 \text{ H}$

$C = 3 \text{ F}$

$V(t) = \sin 2t$

[8]

(d) Draw the phasor diagram of RL, RC and RLC circuit.



Printed Pages – 4

Roll No. :

B028315(028)

**B. Tech. (Third Semester) Examination,
Dec.-Nov. 2021**

(AICTE Scheme)

(Electronics and Telecommunication Engg. Branch)

DATA STRUCTURES USING C++

Time Allowed : Three hours

Maximum Marks : 100

Minimum Pass Marks : 35

Note : Attempt all questions. Every question has four parts. Part (a) is compulsory. Attempt any two parts from (b), (c) and (d).

Unit-I

1. (a) Write the benefits of Object Oriented Programming. 4

[2]

- (b) Define class and object. Explain the use of access specifiers (Public, private and protected with help of example. 8
- (c) What do you mean by friend function? How it is declared, defined and called? Explain with example. 8
- (d) What is Constructor? Explain types of constructor with example. 8

Unit-II

2. (a) Define Virtual base class. 4
- (b) Write a C++ program to overload the '+' operator to add two strings. 8
- (c) Explain function overloading with the help of an example. 8
- (d) Define Inheritance. Explain the differences between Multiple and Multilevel Inheritance. 8

Unit-III

3. (a) Define abstract class. 4

[3]

- (b) Develop a C++ Program to demonstrate the usage of *new* and *delete* operators. 8
- (c) Explain Virtual functions with example. 8
- (d) Write a C++ program demonstrating use of the pure virtual function with the use of base and derived classes. 8

Unit-IV

4. (a) Define Linear Search. 4
- (b) Explain Binary search with the help of a C++ program. Give one example. 8
- (c) Write a program to sort an array of integers using Bubble Sort. Also show the output for following array : 45, 10, 70, 5, 18, 75, 55, 4, 60, 2 8
- (d) Explain how to implement Circular queue and Priority Queue with suitable example. 8

Unit-V

5. (a) Define Linked Lists. 4

[4]

- (b) Describe the implementation of a binary search tree with the help of an example. 8
- (c) Explain sequential representation of graph using 8
- (i) Adjacency matrix
 - (ii) Adjacency list
- (d) Explain BFS and DFS graph traversal techniques with the help of example. 8