

B028313(028)

B.Tech. (Third Semester) Examination

Nov.-Dec. 2020

(New Scheme)

DIGITAL SYSTEM DESIGN

Time Allowed : Three hours

Maximum Marks : 80

Minimum Pass Marks : 28

Attempt all questions. Part (a) is compulsory & Solve any two parts from (b), (c) and (d) of each questions.

Unit-I

- 1. (a) Write the Distributive Laws. 2
- (b) Using Boolean Algebra, prove that : 7
 - (i) $AB + ABC + A\bar{B} = A$

[2]

(ii) $(B + A)(B + D)(A + C)(C + D) = BC + AD$

(iii) $AB + A'C = (A + C)(A' + B)$

(c) Reduce using mapping the following Boolean function
in : 7

(i) Sum of products

(ii) Product of sums

Also implement it using Universal Gates

$$F(A, B, C, D) = \sum m(0, 1, 2, 3, 5, 7, 8, 9, 10, 12, 13)$$

(d) Reduce the following expression using tabular
method. 7

$$F(A, B, C, D) = \sum m(0, 2, 3, 5, 8, 10, 11, 13)$$

Unit-II

2. (a) Differentiate between combinational and sequential
circuits. 2
- (b) Design a Full adder circuit using Decoder. 7
- (c) Draw the neat & clean diagram of BCD Adder and
explain its working through table. 7

B028313(028)

[3]

(d) What is Multiplexer? Write down its application and
draw 16 : 1 multiplexer using only 2 : 1 multiplexer. 7

Unit-III

3. (a) Write difference between Latch and flip-flop. 2
- (b) Draw the logic diagram of J-K flip-flop and explain
its working to : 7
- (i) Obtain the flip-flop characteristics table
- (ii) Obtain characteristics equation
- (iii) Obtain excitation table
- (c) Design BCD Ripple Counter and explain its
functioning. 7
- (d) What is Shift Register? Explain various types of shift
register in brief. 7

Unit-IV

4. (a) Compare Moore & Mealy FSM. 2
- (b) What is Algorithmic State Machines charts? List the
silent features of the ASM charts. 7

B028313(028)


PTO

[4]:

- (c) Design a Pulse train generator using a shift register to generate the following waveform : 7



 - (d) Reduce the number of states in the following state table and tabulate the reduced state table and also draw the reduced state diagram. 7



Unit-V

5. (a) Define Fan-in and Fan-out. 2
- (b) Give comparison among various logic families. 7
- (c) Draw the circuit diagram and explain the operation of 2 inputs TTL NAND gate with totem-pole output. 7
- (d) Draw two input CMOS NAND & NOR gate and explain their operations. 7