

Printed Pages – 4

Roll No. :

B024314(024)

**B. Tech. (Third Semester) Examination,
Nov.-Dec. 2021**

A) CTE (New Scheme)

DIGITAL ELECTRONICS

Time Allowed : Three hours

Maximum Marks : 100

Minimum Pass Marks : 35

Note : Attempt all questions. Part (a) of each question is compulsory. Attempt any two parts from (b), (c) and (d) of each question.

Unit-I

1. (a) What is Parity bit? Explain. 4

(b) (i) Convert gray code 101011 into its binary equivalent. 2

B024314(024)

PTO

[2]

- (ii) Convert $(85.63)_{10}$ to binary. 2
- (iii) Convert $(2AC5.D)_{16}$ to decimal. 2
- (iv) Convert $(475.25)_8$ to decimal. 2
- (c) What is the simplified form of the Boolean expression?
- (i) $ABC' + ABC + A'BC + A'BC'$ 2
- (ii) $(A' + B)(A + B)$ 2
- (iii) $X = B + A \cdot B' + A \cdot B$ 2
- (iv) $(125)_R = (203)_8$, find out the value of radix R. 2
- (d) The message below has been coded in the even parity humming code transmitted through a noise channel. Code the message assuming that it must have a single error occurred in each word code.
(0111001) 8

Unit-II

2. (a) Distinguish between sum-of-products and product-of-sums. 4

B024314(024)

[3]

- (b) Implement the following function with a Multiplexer. 8

$$F(A, B, C, D) = \sum(0, 1, 3, 4, 8, 9, 15)$$

- (c) Simplify the expression given below using K map. 8

$$Y = \sum m(0, 1, 5, 9, 13, 14, 15) + d(3, 4, 7, 10, 11)$$

- (d) Determine the prime - implicants of the function. 8

$$F(W, X, Y, Z) = \sum(1, 4, 6, 7, 8, 9, 10, 11, 15)$$

Unit-III

3. (a) What is basic function flip-flop? 4
- (b) Convert T FLIP-FLOP to D FLIP-FLOP. 8
- (c) Explain JK flip-flop with suitable logic diagram, & explain its operation. 8
- (d) Explain right counter & also explain synchronous counters. 8

Unit-IV

4. (a) Explain digital to analog converter. With suitable example. 4

B024314(024)

PTO

[4]

- (b) Explain weighted resistor/converter. 8
- (c) Describe A/D converter with example. 8
- (d) Explain R-2R Ladder D/A converter. 8

Unit-V

- 5. (a) Explain memory organization. 4
- (b) What is programmable logic array? How it differs from ROM? 8
- (c) Explain classification and characteristics of memories with example. 8
- (d) Explain ROM & also explain types of ROM. 8