

**328413(28)**

**B. E. (Fourth Semester) Examination, 2020**

**(Old Scheme)**

**(EEE, Et & T, IT & Mechatronics Engg. Branch)**

**ANALOG ELECTRONIC CIRCUITS**

*Time Allowed : Three hours*

*Maximum Marks : 80*

*Minimum Pass Marks : 28*

*Note : Part (a) of each question is compulsory and attempt any two part from (b) and (c) of each questions.*

**Unit-I**


1. (a) Which of the transistor configurations has the highest

$R_i$

2

[ 2 ]

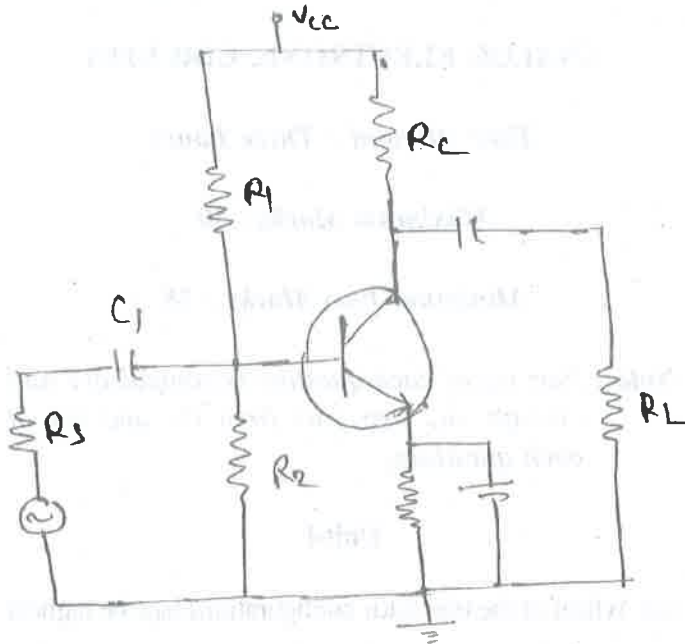- (b) Write a short note on Miller's theorem. 7
- (c) Draw a typical common emitter amplifier and explain the function of each component in it. 7
- (d) Consider a signal stage CE amplifire with  $R_S = 1 \text{ k}\Omega$ ,  $R_1 = 50 \text{ K}$ ,  $R_2 = 2 \text{ K}$ ,  $R_C = 1 \text{ K}$ ,  $R_L = 1.2 \text{ K}$ ,  $h_{fe} = 50$ ,  $h_{ie} = 1.1 \text{ K}$ ,  $h_{oe} = 25 \mu\text{A/V}$  and  $h_{re} = 2.5 \times 10^{-4}$  as show in fig. below



Find  $A_i$ ,  $R_i'$ ,  $A_V$ ,  $A_{is}$ ,  $A_{vs}$ .

7

328413(28)

[ 3 ]

### Unit-II

2. (a) At what frequency short circuit CE current gain becomes unity. 2
- (b) Draw the hybrid  $\pi$  equivalent of a CE transistor valid for high frequency and explain significance of each parameter. 7
- (c) Short circuit CE current gain of transistor is 25 at a frequency of 2 MHz if  $f_p = 200 \text{ kHz}$ . Calculate (i)  $f_T$  (ii)  $h_{fe}$  (iii) find  $|A_i|$  at frequency of 10 MHz and 100 MHz. 7
- (d) Prove that  $h_{fe} = g_m r_{b'e}$ . 7

### Unit-III

3. (a) Define rise time. 2
- (b) What is effect of cascading on fequency response and Band width? 7
- (c) Explain different types distortion occure in amplifiers. 7

328413(28)

PTO

[ 4 ]

- (d) A multistage amplifier is to be constructed using four identical stage, each of which has lower cut-off frequency 15 Hz and upper cutoff frequency 30 kHz.
- (i) What will be lower and upper cutoff frequency of the multistage amplifier?
- (ii) If the mid-band voltage gain of each stage is 8.2, what will be approximate gain of the multistage amplifier at 7.5 Hz and at 300 kHz? 7

#### Unit-IV

4. (a) In which type topology in Negative feedback an amplifier input resistance is increases. 2
- (b) Discuss the advantage and disadvantage of -ve feedback 7
- (c) Give step-by-step procedure for identifying topology of feedback in amplifiers. 7
- (d) An amplifier has mid-band voltage gain ( $A_{vmid}$ ) of 1000 with  $f_L = 50$  Hz and  $f_H = 50$  kHz, if 5% feedback is applied then calculate gain,  $f_{LF}$  and  $f_{HF}$  with feedback. 7

[ 5 ]

#### Unit-V

5. (a) What is the Barkhausen criterion for the feedback oscillators? 2
- (b) Draw a neat circuit diagram of a phase shift oscillator using BJT and an expression for its frequency of oscillations. 7
- (c) Draw the wein bridge oscillator using BJT. Show that the gain of the amplifier must be at least 3 for oscillation to occur. 7
- (d) Explain the working of Colpitts oscillator and state the formula for the frequency. 7