

328414(28)

B. E. (Fourth Semester) Examination, 2020

(Old Scheme)

(AEI, EEE, EI, Et & T Branch)

DIGITAL ELECTRONIC CIRCUITS

Time Allowed : Three hours

Maximum Marks : 80

Minimum Pass Marks : 28

Note : Attempt all questions. Part (a) from each question is compulsory & carries 2 marks each. Attempt any two parts from (b), (c) and (d) of each question & carries 7 marks each.

Unit-I

1. (a) Why and which code is used for labelling the cells of K map?

[2]

- (b) Assume that the data has been encoded in a 7-bit even parity Hamming code and the number 1011011 is received. Find out the bit in error. What will be the corrected code be?
- (c) State the method for Binary to Gray & Gray to binary code conversion with suitable example?
- (d) State De-Morgan's theorem & prove it?

Unit-II

2. (a) Find and min term for $BC + A$.
- (b) Simplify using K-map and implement it with NAND gate :

$$F = \sum m(0, 1, 2, 3, 4, 5, 10, 11)$$

- (c) Simplify the Boolean function F in the POS form using tabulation method.

$$F(A, B, C, D) = \sum(3, 4, 5, 9, 14) \\ + d(7, 13, 15)$$

- (d) Explain Quine-Mcclusky Method in detail with suitable example?

328414(28)

[3]

Unit-III

3. (a) What is PAL and PLA?
- (b) Design a 4-bit BCD adder circuit?
- (c) Construct a 4×16 decoder using 3×8 decoder?
- (d) Explain how multiplexer is used as universal function generator?

Unit-IV

4. (a) What is Sequential circuit?
- (b) Design J-K flip flop using S-R flip-flop?
- (c) Draw and explain working of parallel in serial out (PISO) register. Explain how a number can be shifted in and out from such a register?
- (d) Design a synchronous Decode counter?

Unit-V

5. (a) What is tristate logic?
- (b) Give comparison among various logic families.
- (c) Define following parameter's :
- (i) Current and voltage

328414(28)

PTO

[4]

- (ii) Noise Margin
 - (ii) Propagation delay
 - (iii) Power dissipation
 - (iv) Speed power product
- (d) Explain TTL in detail.