

Printed Pages – 7

Roll No. :

324453(25)

B. E. (Fourth Semester) Examination, 2020
APR-MAY 2022
(New Scheme)

Elect **(EE Engg. Branch)**

NETWORK ANALYSIS & SYNTHESIS

Time Allowed : Three hours

Maximum Marks : 80

Minimum Pass Marks : 28

Note : Attempt all questions. Part (a) of each question is compulsory and carries 2 marks each and attempt two parts from (b), (c) and (d) carrying 7 marks each.

Unit-I

1. (a) Define Ramp and impulse functions.


2

| 2 |

(b) In the network of fig shown below, the switch is changed from the position a to b on $t = 0$. Solve for

$$i, \frac{di}{dt} \text{ and } \frac{d^2i}{dt^2} \text{ at } t = 0^+.$$


7

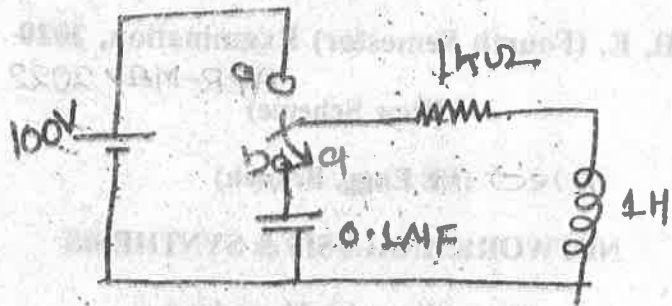

(c) In the network of figure shown below, the switch is open for a long time and at $t = 0$, it is closed.

Determine $v_2(t)$.


7

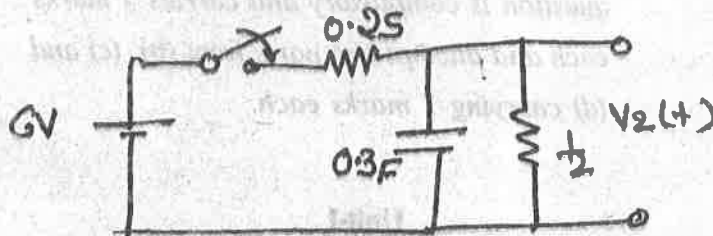

| 3 |

(d) Find the Laplace transform of the waveform shown in fig.

7

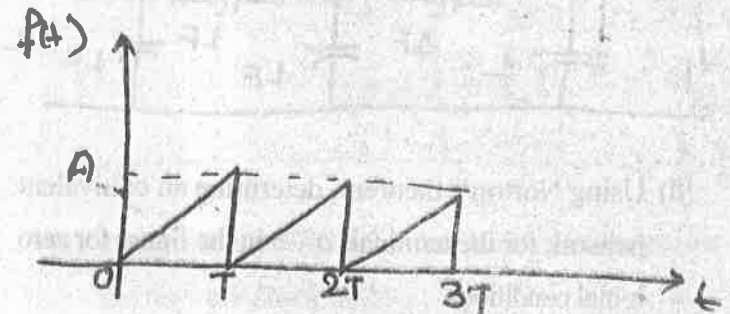

Unit-II

2. (a) Define driving point function. 2


(b) Discuss the restriction locating the poles and zeros of a driving point function in s-plane. 7

(c) For the network shown in the figure, show that the voltage-ratio transfer function is


$$G_{12} = \frac{(s^2 + 1)^2}{5s^4 + 5s^2 + 1}$$

7

[4]

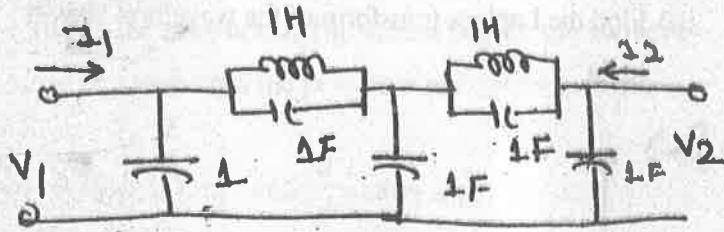

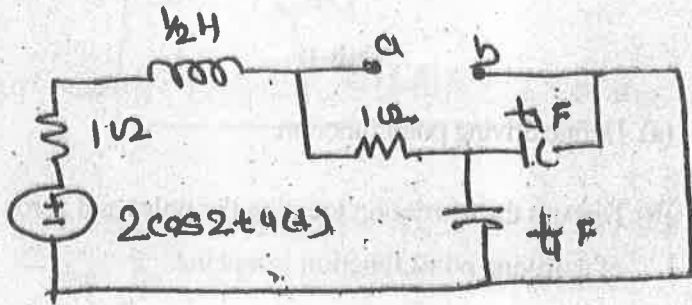
- (d) Using Norton's theorem, determine an equivalent network for the terminals $a - b$ in the figure for zero initial conditions. 7




Unit-III

3. (a) Explain Bartlett's bisection theorem. 2
- (b) The accompanying network contains a voltage controlled source and a current controlled source. For the element values specified, determine the Y and Z parameters. 7

[5]

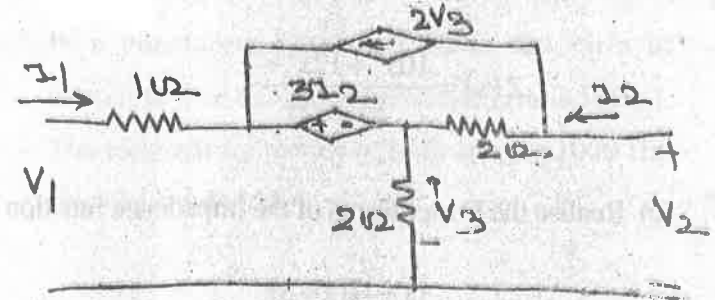

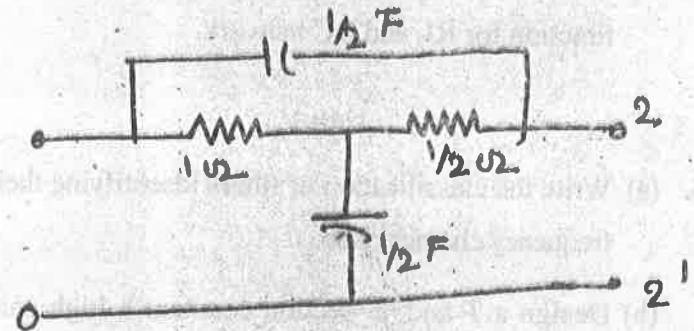- (c) Determine the $ABCD$ (transmission) parameters for the network show below. 7



- (d) Obtain the z -parameters in terms of h -parameters. 7

Unit-IV

4. (a) What are the properties of positive real functions? 2
- (b) Realise the Cauer forms of the following LC impedance function : 7

[6]

$$Z(s) = \frac{10s^4 + 12s^2 + 1}{2s^3 + 2s}$$

- (c) Realise the Foster forms of the impedance function : 7

$$Z(s) = \frac{(s+1)(s+3)}{s(s+2)}$$

- (d) Explain the properties of driving point immittance function for RL and RC network. 7

Unit-V

5. (a) Write the classification of filters identifying their frequency characteristic. 2
- (b) Design a T and π section constant-k high pass filter having cut-off frequency of 12 kHz and nominal impedance $R_0 = 500\Omega$. Also find its characteristic impedance and phase constant at 24 kHz. 7
- (c) Derive the expression for characteristic impedance of π -type low pass filter. Also prove that

$$Z_{0r} = \sqrt{Z_{sc} \times Z_{oc}} \quad 7$$

[7]

- (d) In a constant-k band-pass filter, the ratio of capacitance in the shunt and series arm is 100 : 1. The resonant frequency of both arms is 1000 Hz. Find the bandwidth. 7