

324453 (25)

BE (4th Semester)

Examination, Nov.-Dec., 2021

Branch : Elect.

**NETWORK ANALYSIS &
SYNTHESIS (NEW)**

Time Allowed : Three Hours

Maximum Marks : 80

Minimum Pass Marks : 28

Note : Part (a) of each question is compulsory. Attempt any two from (b), (c), (d).

Unit-I

Q. 1. (a) Represent mathematically and graphically the following continuous time signals : 2


(i) Unit step

(ii) Ramp

(iii) Impulse

(2)

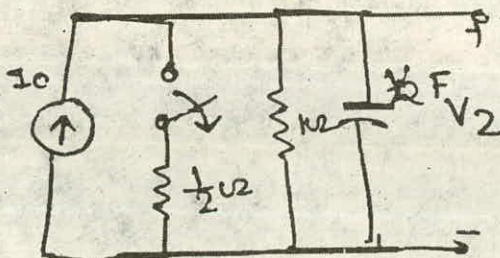
- (b) For the circuit shown in fig., find the voltage across the $1\ \Omega$ resistor when the switch S is opened at $t = 0$. Assume there is no charge on the capacitor and no current in the inductor before switching.




- (c) For the fig shown below, the switch S is in position a for long time and moved to position B at $t = 0$. Obtain the values of i_L , V_C and their first derivatives at $t = 0^+$.

324453 (25)

(3)

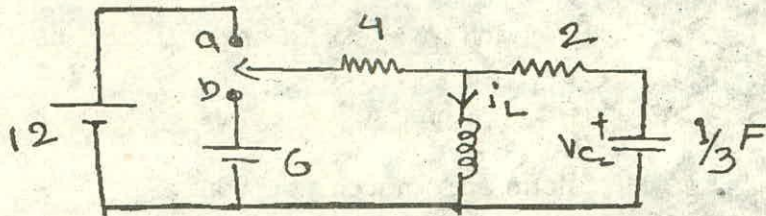

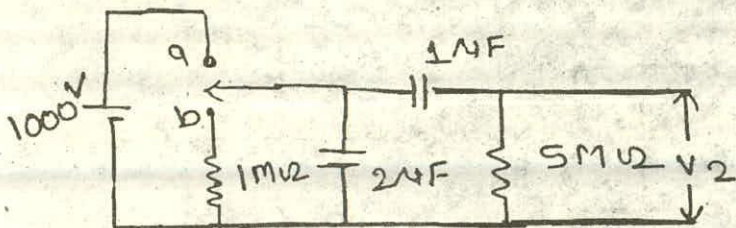- (d) With switch k in position a , the network shown attain equilibrium. At time $t = 0$, the switch is moved to position b . Find the voltage across R_2 as a function of time. 7




Unit-II


- Q. 2. (a) Define all the transfer functions of the two port network ? 2

(4)

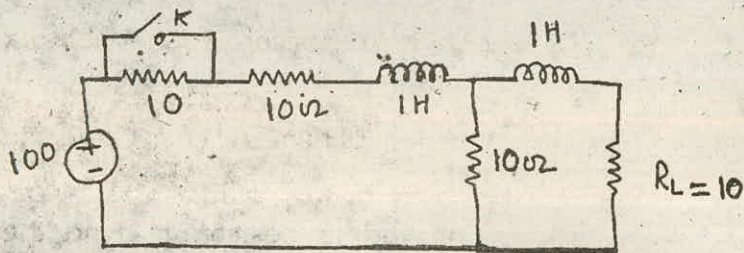- (b) If the switch 'k' is closed at $t = 0$, find the current $i(t)$ through R_L by using Laplace transform and Thevenin's theorem. 7



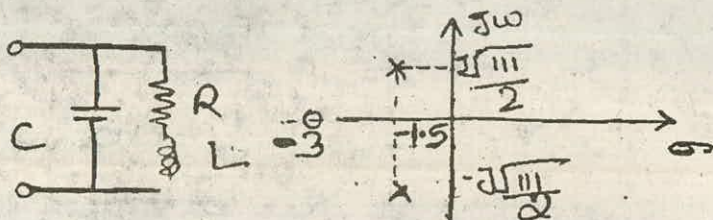- (c) The network and its pole zero plot of $z(s)$ is shown in fig. 7




The impedance has the form

$$z(s) = \frac{k(s - z_1)}{(s - p_1)(s - p_2)}$$

If $z(j\omega) = 1$, find the values of R , L and C .

(5)

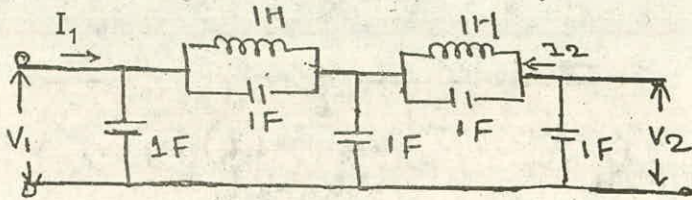
(d) For the network shown, find the voltage gain. 7



Unit-III


Q. 3. (a) Draw the equivalent circuit of a 2-port network in terms of z parameters. 2

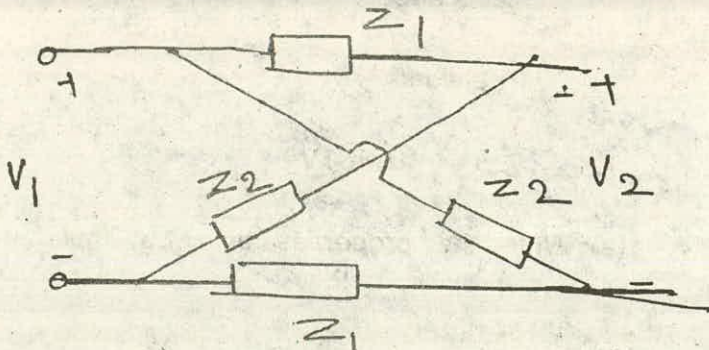(b) Find z parameter for the reciprocal and symmetric two-port network shown below. 7



(6)

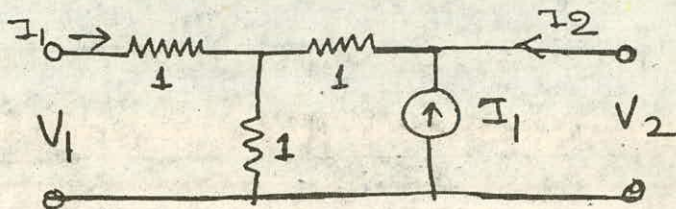- (c) Find 'y' parameters. State whether the network is symmetrical and reciprocal. 7



- (d) (i) For a network to be reciprocal show that $AD - BC = 1$. Where A, B, C and D are the transmission parameters. 3
- (ii) Derive the condition (or result) for cascaded connection of two port networks. 4

Unit-IV

- Q. 4. (a) Write the properties of R-Lb impedance functions. 2


(7)

(b) (i) Determine the range of β such that the polynomial 4

$$P(s) = s^4 + s^3 + 4s^2 + \beta s + 3 \text{ is Hurwitz}$$

(ii) Define the positive real function and mention its properties. 3

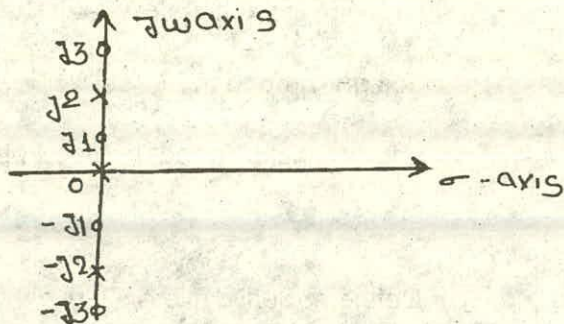(c) An impedance function has the pole zero pattern shown below. If $z(-2) = -\frac{130}{16}$, synthesize the impedance in Foster II forms. 7



(d) An impedance function is given by

$$Z(s) = \frac{s(s+2)(s+5)}{(s+1)(s+4)}$$

Find the R-L presentation

of Cauer-I and II forms. 7

(8)

Unit-V

- Q. 5. (a) Define all the parameters of a filter. 2
- (b) A T-section low pass filter has series inductance 80 mH and shunt capacitance $.022 \mu\text{F}$. Determine the cut-off frequency and nominal design impedance. Also design an equivalent π -section. 7
- (c) Design a T-section constant k-high pass filter having cutoff frequency of 10 kHz and design impedance of 600Ω . Find its characteristic impedance and phase constant at 25 kHz. 7
- (d) Define m-derived filters. Derive the expressions of m-derived band-pass filters. 7