

**328453 (28)**

BE (4<sup>th</sup> Semester)

Examination, Nov.-Dec., 2021

Branch : Et & T

**ANALOG ELECTRONICS (NEW)**

*Time Allowed : Three Hours*

*Maximum Marks : 80*

*Minimum Pass Marks : 28*

**Note :** Part (a) of each question is compulsory. Attempt any two parts from part (b), (c) & (d) of each question. Part (a) is of 2 marks and Part (b), (c) & (d) are of 7 marks each. Symbols have their usual meanings.

(2)

Q. 1. (a) What is biasing problem in a common collector circuits and how this problem is overcome ? (In brief).

(b) The transistor amplifier shown in figure (1) uses a transistor whose h-parameters are given as :

$h_{ie} = 1.1 \text{ K}$ ,  $h_{fe} = 50$ ,  $h_{re} = 2.5 \times 10^{-4}$  and  $h_{oe} = 24 \mu\text{A/V}$ . Calculate  $A_I = I_o/I_i$ ,  $A_V$ ,  $A_{V_S}$ , and  $R_i$ .

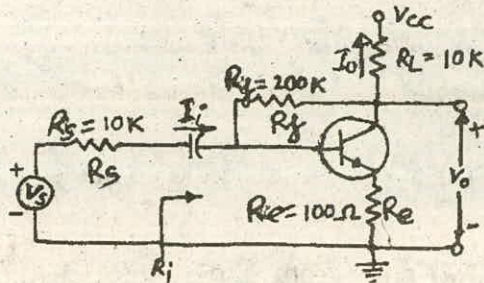


Figure (1)

(c) For the circuit shown in figure (2), verify that

the modified h-parameters are :

$$h'_{ie} = h_{ie} + \frac{(1+h_{fe})R_e}{1+h_{oe}R_e} \text{ and } h'_{re} = \frac{h_{re} + h_{oe}R_e}{1+h_{oe}R_e}$$

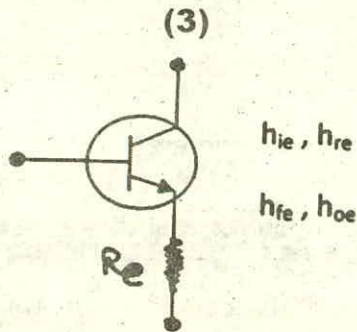


Figure (2)

(d) What is a Darlington pair ? Write its main characteristics. Derive expression for current gain  $A_i$  and input resistance  $R_i$  for a Darlington Pair.

Q. 2. (a) Why h-parameter model is not used to model BJT at high frequencies ?

(b) For hybrid- $\pi$  model derive expression for :

- conductance  $g_{b'e}$
- feedback conductance  $g_{b'c}$
- base spreading resistance  $r_{bb'}$

(4)

- output conductance  $g_{ce}$ ; in terms of h-parameters

(c) The hybrid- $\pi$  parameter of the transistor

- used in the circuit shown in figure (3) are  $g_m = 50 \text{ mA/V}$ ,  $r_{b'e} = 1 \text{ K}\Omega$ ,  $r_{b'c} = 4 \text{ M}\Omega$ ,  $r_{ce} = 80 \text{ K}\Omega$ ,  $C_c = 3 \text{ pF}$ ,  $C_e = 100 \text{ pF}$  and  $r_{bb'} = 100 \Omega$ .

Find (i) Upper 3 dB frequency of current gain

$A_i = I_L/I_i$  (ii) The value of voltage gain  $|A_{V_s}| =$

$|V_o/V_s|$  at frequency of part (i).

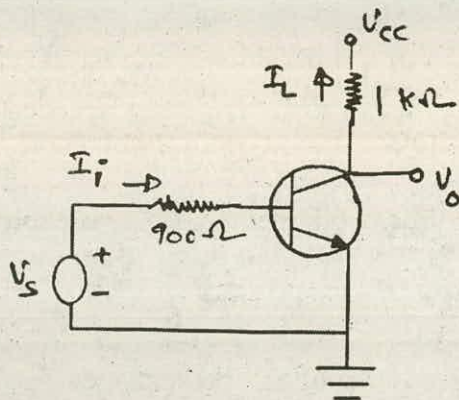


Figure (3)

(5)

- (d) Derive the expression for CE gain-bandwidth product for voltage and current is respectively, as :

$$|A_{V_{so}} f_{HV}| = \frac{f_T}{1 + 2\pi f_T C_C R_L} \frac{R_L}{(R_s + T_{bb'})}$$

$$|A_{I_{so}} f_{HI}| = \frac{f_T}{1 + 2\pi f_T C_C R_L} \frac{R_s}{(R_s + T_{bb'})}$$

- Q. 3. (a) The dynamic transfer characteristic curve for a given transistor is :

$i_C$  (in mA) =  $50 i_b + 1000 i_b^2$ , where  $i_b = 50 \cos 2\pi (100)t$  (in mA). Calculate the percent harmonic distortion.

- (b) Calculate  $C_c$  for  $f_L = 15$  Hz for circuit shown in figure (4).

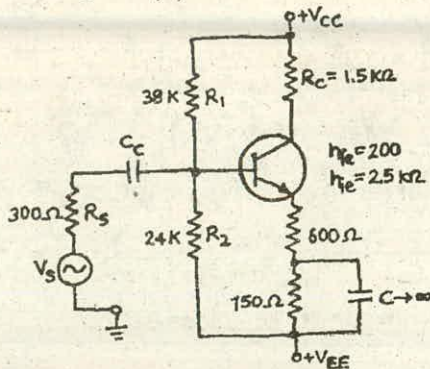


Figure (4)

(6)

- (c) For the cascaded amplifier shown in figure (5), calculate the overall upper 3 dB frequency. Assume that the cascaded stages are non-interacting.



Figure (5)

$$\text{Given } A_{v1} = \frac{A_{vo1}}{1 + \frac{s}{\omega_{H1}}} \text{ and } A_{v2} = \frac{A_{vo2}}{1 + \frac{s}{\omega_{H2}}}$$

where  $A_{vo1}$  and  $A_{vo2}$  are midband gain of amplifier 1 and 2 respectively.  $\omega_{H1} = 2\pi \times 100 \times 10^3$  rad/sec and  $\omega_{H2} = 2\pi \times 500 \times 10^3$  rad/sec and  $S = j\omega$ .

- (d) What is harmonic distortion? How even harmonics are eliminated by Push-Pull arrangement of class-A power amplifier? Explain with circuit diagram.

(7)

- Q. 4. (a) An amplifier having an open-loop gain of 100 is connected in a negative feedback configuration with a feedback factor of 0.1, what is the closed loop gain of the amplifier ?
- (b) Show that bandwidth of an amplifier increases by employing negative feedback.
- (c) For the circuit shown in figure (6),  $A = -1000$ ,  $\beta = V_f/V_o = 1/100$ ,  $R_s = R_e = R_c = 1 \text{ k}\Omega$ ,  $h_{ie} = 1 \text{ k}\Omega$ ,  $h_{fe} = 100$  and  $h_{re}$ ,  $h_{oe}$  are negligible. Find (i)  $V_i$  as a function of  $V_s$  and  $V_f$  (Assume that the inverting amplifier input resistance is infinite.), (ii)  $A_{vf} = V_o/V_s = A V_i/V_s$ .

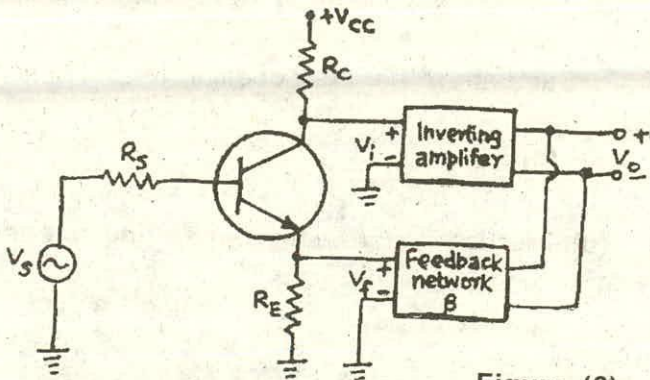


Figure (6)

(8)

(d) Derive the expression for input and output resistance ( $R_{if}$  and  $R'_{of}$ ) with feedback for voltage series topology.

Q. 5. (a) Write Barkhausen criteria for oscillations.

(b) The gain of a forward amplifier is frequency

dependent and given by  $A = \left[ \frac{-9 \times 10^6}{j\omega} \right]$ . If

the feedback fraction is  $\left[ \frac{6 \times 10^3}{(3 \times 10^3 + j\omega)^2} \right]$ ,

find the frequency of oscillations.

(c) Draw basic circuit of Wein bridge oscillator

and show that the condition for oscillation is

$$|A| \geq 3.$$

(d) Discuss factors which affect the frequency

stability of oscillators.