

Printed Pages – 6

Roll No. :

B028412(028)

**B. Tech. (Fourth Semester) Examination,
Nov.-Dec. 2021**

AICTE (New Scheme)

(Electronics & Telecommunication Engineering Branch)

ANALOG CIRCUITS

Time Allowed : Three hours

Maximum Marks : 100

Minimum Pass Marks : 35

Note : All questions are compulsory. Part (a) of each question is compulsory and carries 4 marks. Attempt any two parts from (b), (c) and (d) from each question which carry 8 marks each.

Unit-I

1. (a) State & prove Miller's theorem.

4

B028412(028)

PTO

[2]

(b) Give analysis of a transistor amplifier using h-parameters and obtain the expression for following :

(i) Current gain

(ii) Voltage gain

(iii) Input resistance

(iv) Output resistance

8

(c) For amplifier shown below in fig. 1, calculate R_i ,

R_i' , A_v , A_{vs} and $A_I' = -I_2/I_1$. The transistor para-

meters are $h_{ie} = 1100 \Omega$, $h_{re} = 2.5 \times 10^{-4}$, $h_{fe} = 50$,

$h_{oe} = 24 \mu A/V$.

8

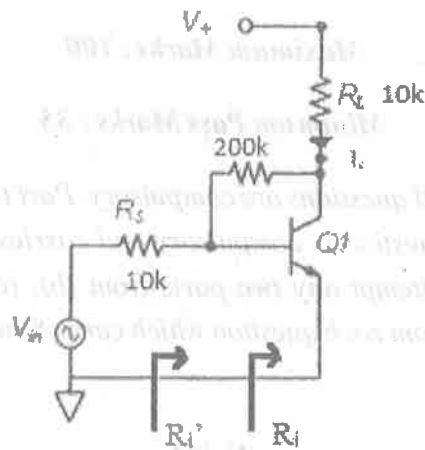


Fig. 1

B028412(028)

[3]

(d) What is Darlington pair circuit? Drive expression for A_I and R_i for such a pair.

8

Unit-II

2. (a) Why h parameter model is not suitable for high frequency signals? Draw the small signal high frequency CE model of transistor.

4

(b) Derive the expression for following hybrid π -model parameters :

8

(i) $r_{b'e}'$ in terms of h -parameters

(ii) r_{bb}' in terms of h -parameters

(iii) $r_{b'c}'$ in terms of h -parameters

(iv) Transconductance gain g_m

(c) The following transistor measurement are made at $I_C = 5 \text{ mA}$, $V_{CE} = 10 \text{ V}$ and at room temperature

$$h_{ie} = 600 \Omega, h_{fe} = 100$$

$$|A_e| = 10 \text{ at } 10 \text{ MHz} \quad C_C = 3 \text{ PF}$$

Find β cut-off frequency (F_β), gain bandwidth

product (F_T), C_e , $r_{b'e}'$ and r_{bb}' .

8

B028412(028)

PTO

[4]

- (d) Derive the expression of f_H for emitter follower at high frequency. 8

Unit-III

3. (a) Define Rise time in multistage amplifiers. How it is related with upper 3 dB frequency of the amplifiers? 4
- (b) Compare the three types of coupling in multistage amplifiers. 8
- (c) What is the effect on band pass when several identical amplifiers are cascaded in series? Drive the expression for overall upper and lower 3 dB frequency. Assume non-interacting stages. 8
- (d) An amplifier consist of 3 identical stages in cascade, the bandwidth of overall amplifier extends from 20 Hz to 20 MHz. Calculate the bandwidth of individual stage. 8

Unit-IV

4. (a) What do you mean by negative feedback? List the characteristics of negative feedback amplifier. 4

[5]

- (b) Derive the derivation of input resistance output resistance of voltage shunt feedback amplifier. 8
- (c) Explain different feedback topologies in detail. 8
- (d) The transistor shown in fig. 2 has the following parameter's : $h_{ie} = 1.1 \text{ k}\Omega$, $h_{fe} = 50$ and $h_{re} = h_{oe} = 0$. Calculate A_{vf} , R_{if} and R'_{of} . 8

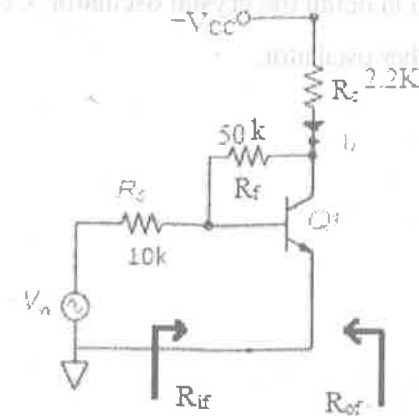


Fig. 2

Unit-V

5. (a) What is the Barkhausen Criterion for the feedback oscillator? 4

[6]

(b) What is $R - C$ phase shift oscillator? Derive the

expression $f = \frac{1}{2\pi RC\sqrt{6+4k}}$; $k = \frac{R_c}{R}$. 8

(c) Draw the circuit of Wien Bridge oscillator and explain its working principle. Drive the expression for frequency of oscillations. 8

(d) Explain in detail the crystal oscillator. Compare it with other oscillator. 8

