

Printed Pages– 5

Roll No. ....

**328551(28)**

**B. E. (Fifth Semester) Examination,  
April-May/Nov. Dec. 2020**

**(New Scheme)**

**(Et & T Engg. Branch)**

**LINEAR INTEGRATED CIRCUITS & APPLICATIONS**

***Time Allowed : Three hours***

***Maximum Marks : 80***

***Minimum Pass Marks : 28***

***Note : Attempt all questions. Part (a) of each question is compulsory. Attempt any two parts from (b), (c) and (d) of each question. The figures in the right-hand margin indicate marks.***

1. (a) What do you mean by Input Offset voltage? Why there is a need to compensate for the same? 2


**328551(28)**

**PTO**

[ 2 ]

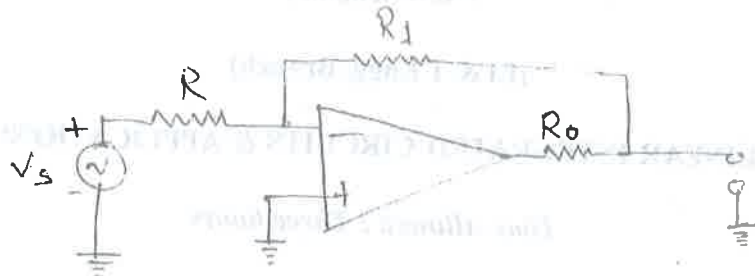- (b) Amplification factor in voltage shunt feedback amplifier is voltage gain. Justify with appropriate circuit diagram and mathematical analysis? 7
- (c) For the circuit shown with  $R_f = \infty$ , show that 7

$$Y_{of} = \frac{1}{R_o} \left[ 1 - A_v \cdot \frac{R_f}{R + R_f} \right] + \frac{1}{R + R_f}$$



- (d) For an op-amp the values of  $R_F$  and  $R_1$  are  $100 \text{ k}\Omega$  and  $1 \text{ k}\Omega$  respectively. It is an inverting amplifier with input offset voltage drift of  $14 \mu\text{V}/^\circ\text{C}$  and input offset current drift of  $0.5 \text{ nA}/^\circ\text{C}$ . The amplifier is nulled at  $25^\circ\text{C}$ . Evaluate the error voltage and the output at  $45^\circ\text{C}$  if input is  $1 \text{ mVdc}$ . 7

328551(28)


[ 3 ]

2. (a) Draw the circuit diagram of an ideal integrator op-amp and write expression for output. 2
- (b) Design a Schmitt trigger circuit with the help of op-amp. Explain how it eliminates comparator chatter? 7
- (c) Define a three op-amp instrumentation amplifier to vary gain from 1 to 10,000. 7
- (d) The circuit shown is a differential amplifier using an ideal op-amp : 7
- (i) Find the output voltage  $V_o$ .
- (ii) Show that the output corresponding to  $V_c = \frac{1}{2}(V_1 + V_2)$  is equal to zero if  $\frac{R_1}{R} = \frac{R_3}{R_2}$  find output voltage in this case.
- (iii) Find the common mode rejection ratio of amplifier if  $\frac{R_1}{R} \neq \frac{R_3}{R_2}$

328551(28)

PTO

[ 4 ]

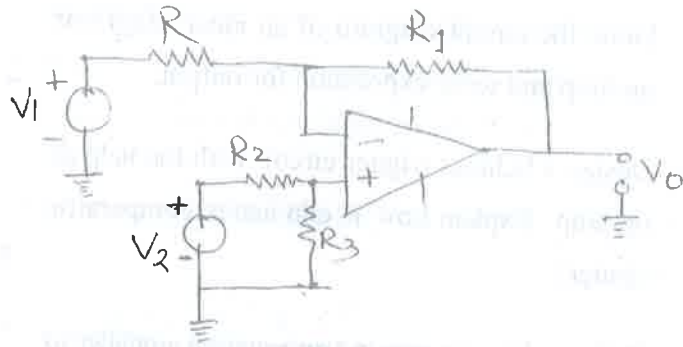

3. (a) Define resolution of DAC. 2
- (b) What are important specifications required for designing Analog to Digital converter. 7
- (c) Draw circuit diagram of Dual slope ADC and explain how an analog signal is converted to Digital signal? 7
- (d) Draw neat diagram for 4-bit R-2R ladder D/A converter and weighted resistor type D/A converter. Compare them? 7
4. (a) Define safe operating area. 2
- (b) Differentiate between series and shunt op-amp voltage regulator? 7

[ 5 ]

- (c) Explain short circuit protection and foldback current limiting with characteristic for a voltage regulator. 7
- (d) Draw the experimental setup block diagram and circuit diagram to convert 230V AC 50 Hz supply into 5 V DC supply using 78XX series IC. Also explain each and every stage in brief. 7
5. (a) What do you mean by lock range and capture range? 2
- (b) Draw and explain the block diagram of PLL? 7
- (c) Discuss application of PLL circuits in AM detection? 7
- (d) Draw and explain the block diagram of PLL? 7