

Printed Pages – 5

Roll No. : .....

**328511(28)**

**B. E. (Fifth Semester) Examination, April-May 2021**

**(Old Scheme)**

**(EEE, Et&T Engg. Branch)**

**LINEAR INTEGRATED CIRCUITS  
& APPLICATIONS**

***Time Allowed : Three hours***

***Maximum Marks : 80***

***Minimum Pass Marks : 28***

***Note : Part (a) of each question is compulsory.***

***Attempt any two parts (b), (c) and (d).***

**Unit-I**

1. (a) Draw equivalent circuit of an OP-AMP. 2
- (b) Derive the expression for output resistance of a non inverting configuration of OP-AMP. 7

**328511(28)**

**PTO**

[ 2 ]

- (c) What is slew rate? List causes of the slew rate and explain its significance in application. 7
- (d) The following specifications are given for the dual input, balanced output bipolar differential amplifier : 7

$$R_e = 2.2 \text{ K}\Omega, V_{EE} = -10 \text{ V}$$

$$R_E = 4.7 \text{ K}\Omega, \beta_F = \beta_0 = 100$$

$$R_s = 50 \Omega$$

$$V_{cc} = 10 \text{ V}$$

Assume  $V_{BE} = 0.7 \text{ V}$ . Determine the following :

- (i)  $I_{CQ}$  and  $V_{CEQ}$
- (ii) Differential mode voltage gain
- (iii) Input and output resistance

### Unit-II

2. (a) Draw circuit diagram for the given equation. 2

$$V_o = V_A - V_B$$

- (b) Explain logarithmic amplifier and also show that output voltage  $V_o$  of logarithmic amplifier is : 7

328511(28)


[ 3 ]

$$V_o = \frac{-KT}{q} \ln \left( \frac{V_i}{R_1 I_0} \right)$$

- (c) Design an OP-AMP schmitt trigger for the following specifications : 7

$$V_o = \pm 10 \text{ volts, tripping voltages } 4 \text{ V and } -2 \text{ V}$$

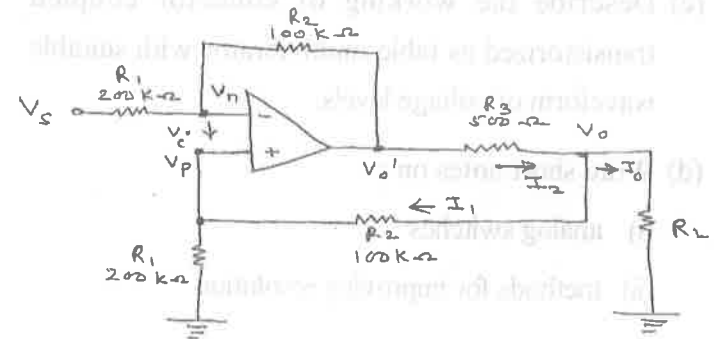- (d) In the voltage controlled current source shown in the below figure an output current,  $I_o = 10 \text{ mA}$  is desired. Calculate  $V_o$ . 7



### Unit-III

3. (a) Write different types of clamping circuits. 2
- (b) Explain how high pass filter act as differentiator. 7

328511(28)

PTO

[ 4 ]

- (c) Draw and explain low pass RC circuit as integrator, also explain what are the advantages of low pass RC integrator over basic integrator. 7
- (d) Draw the circuit for voltage sweep generator and explain. 7

**Unit-IV**

4. (a) Write the need of commutating capacitors. 2
- (b) Explain different types of multivibrators with their applications. 7
- (c) Describe the working of collector coupled transistorized astable multivibrator with suitable waveform of voltage levels. 7
- (d) Write short notes on : 7
- (i) analog switches
  - (ii) methods for improving resolution

**Unit-V**

5. (a) Calculate the output pulse width if  $R = 10 \text{ k}\Omega$ ,  $C = 0.1 \mu\text{F}$  are connected in monostable circuits. 2

[ 5 ]

- (b) Draw and explain functional block diagram of LM 723 high precision voltage regulator. 7
- (c) Design an astable multivibrator using 555 timer with 50% duty cycle. 7
- (d) Draw and explain block diagram and pin functions of IC 555. 7