

Printed Pages – 5

Roll No. :

328612(28)

B. E. (Sixth Semester) Examination, April-May 2021

(Old Scheme)

(Et&T Engg. Branch)

ADVANCED ELECTRONIC CIRCUITS

Time Allowed : Three hours

Maximum Marks : 80

Minimum Pass Marks : 28

Note : Attempt all questions. Part (a) is compulsory from each question. Attempt any two parts from (b), (c) and (d).

Unit-I


1. (a) What is the advantage of inverted R – 2R DAC over R – 2R DAC ladder network? 2

[2]

- (b) Draw and explain the circuit of dual slope Analog to Digital converter in detail. 7
- (c) Draw & explain the diagram of Delta Modulation type Analog to Digital converter. 7
- (d) A 10 bit Digital to Analog converter has a step size of 10 mV. Determine the full scale output voltage and its percentage resolution. 7

Unit-II

 2. (a) Explain the meaning of bilinear Transfer function. 2
- (b) Design a filter for the plot given below and determine half power frequency. 7




[3]

- (c) Write down different steps for designing of inverting opamp and non inverting op-amp. How can we analyse the necessity of the filter? 7
- (d) What is the need to add fourth opamp in biquad circuit & also derive the expression of four opamp biquad circuit with frequency response. 7

Unit-III

3. (a) Explain RC – CR transformation. 2
- (b) Design a low pass Butterworth Response from the given specifications $\alpha_{\max} = 0.5 \text{ db}$, $\alpha_{\min} = 30 \text{ db}$, $K = A_0 = 1$, $w_p = 750 \text{ rad/sec}$, $w_s = 1750 \text{ rad/sec}$, use scaling in the final design. 7
- (c) Explain with circuit diagram the working of Deyliannis-Friend's circuit. 7
- (d) The following specifications are given for a Chebyshev low pass filter : $w_p = 1 \text{ rad/sec}$, $w_s = 2.33 \text{ rad/sec}$, $\alpha_{\max} = 0.5 \text{ db}$ and $\alpha_{\min} = 22 \text{ db}$ design a filter. 7

[4]

 

Unit-IV

4. (a) Define Lock Range and Capture Range. 2
- (b) A PLL has a VCO with $K_0 = 25 \text{ kHz/V}$ and $f_c = 50 \text{ kHz}$. The amplifier gain is $A = 2$ and the phase detector has a maximum output voltage swing of $\pm 0.7 \text{ V}$. Find the lock range of PLL. Assume filter gain to unity. 7
- (c) Explain the operation of IC 565 VCO and explain its operation. 7
- (d) Derive the expression for lock range & capture range of phase locked loop. 7

Unit-V

5. (a) What is the mean of Quadrant of multiplier? 2

[5]

- (b) Draw & explain the working of logarithmic multiplier. 7
- (c) Write the application of multiplier circuit & explain multiplier as phase detector. 7
- (d) Explain how to get square root and square of the given analog signal? 7