

Printed Pages – 6

Roll No. : .....

**328652(28)**

**B. E. (Sixth Semester) Examination, April-May 2021**

**(New Scheme)**

**(Et & T Branch)**

**ELECTRONIC CIRCUIT DESIGN**

***Time Allowed : Three hours***

***Maximum Marks : 80***

***Minimum Pass Marks : 28***

***Note : Attempt all questions. Part (a) is compulsory and carries 2 marks and, attempt any two from part (b), (c) & (d) and carries 7 marks.***


**Unit - I**

1. (a) Calculate oscillation frequency of the square wave generator where  $R = 10k\Omega$  and  $C = 0.01 \mu F$ .  
(b) Draw the circuit of Triangular wave generator using

[ 2 ]

OPAMP and explain its operation.

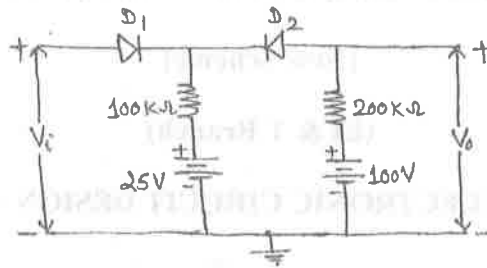- (c) The input voltage  $V_i$  to the two level clipper shown in figure varies linearly from 0 to 150 volt. Sketch the output voltage  $V_o$  to the same time scale as the input voltage. Assume ideal diodes.



- (d) Draw and explain current sweep generator in details.

### Unit - II

2. (a) What is a multivibrator? Give the names of different types of multivibrator.
- (b) With the help of a schematic diagram explain how the commutating capacitor reduces the transition time.
- (c) The fixed-bias binary shown in figure uses n-p-n

328652(28)


[ 3 ]

silicon transistor with  $V_{CE(sat)} = 0.5V$ ,

$V_{BE(sat)} = 1V$ ,  $I_{CBO} = 10nA$  at  $25^\circ C$  and zero base to emitter voltage at cut-off. The circuit parameters are  $V_{CC} = V_{BB} = 6V$ ,  $R_C = 1.2k\Omega$ ,

$R_1 = 4.7k\Omega$ ,  $R_2 = 27k\Omega$ . Find :

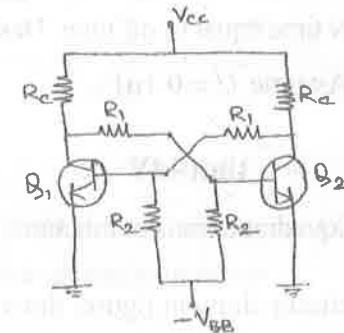- (i)  $h_{FE}$  (min) and stable state voltages and currents.
- (ii) If the reverse saturation current doubles for every  $10^\circ C$  rise in temperature, what is the maximum temperature at which the circuit can operate properly with one device remaining off?



- (d) Draw and explain schmitt trigger circuit. Write

328652(28)

PTO

[ 4 ]

some applications of this circuit.

### Unit - III


3. (a) Why normally control terminal of IC-255 timer is connected to ground through  $0.01 \mu\text{F}$  by pass capacitor?
- (b) With neat circuit diagram explain astable multivibrator using IC-555. Also derive the relation for its duty cycle.
- (c) Discuss how monoshot can be used as missing pulse detector?
- (d) Design an astable multivibrator which will flash an electric bulb such that its on time will be 3 second and off time will be 1 second. Modify the circuit to get ON time equal to off time. Design both the circuits. Assume  $C = 0.1 \mu\text{F}$ .

### Unit - IV


4. (a) Define Biquadratic transfer function.
- (b) For the circuit show in figure, draw asymptotic Bode plot for magnitude  $T(3\omega)$ .

328652(28)

[ 5 ]

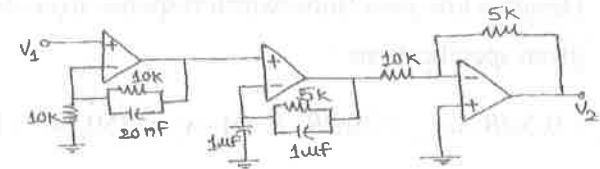

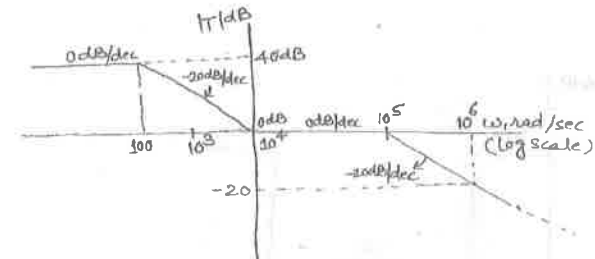- (c) Explain Biquad circuit with circuit diagram and also derive an expression for frequency response.
- (d) The accompanying figure shows the asymptotic Bode plot for a desired magnitude response. Design an amplifier filter using a minimum number of OPAMP. Give the schematic and indicate the element values for your design.



### Unit - V

5. (a) Differentiate Butterworth filter and Chebyshev filter relative to attenuation factor.
- (b) Define sensitivity. Explain the sensitivity analysis of sallen and key circuit.

328652(28)

PTO

[ 6 ]

(c) Design a low pass Butterworth response from the given specifications :

$$\alpha_{\max} = 0.5 \text{ dB}, \alpha_{\min} = 30 \text{ dB}, K = 1, \omega_p = 750, \omega_s = 1750$$

use scaling in final design.

(d) Design a bandpass filter to meet the specification shown in figure with the added requirement that the response be Butterworth. It is required that

$\alpha(2000) = 0$ . Show steps in the Geffe algorithm carefully. In your final design, at least one capacitor should have the value of  $0.1 \mu\text{F}$ .

