

Printed Pages – 3

Roll No. :

328654(28)

B. E. (Sixth Semester) Examination Nov.-Dec. 2021

(New Scheme)

(Et&T Branch)

VLSI DESIGN

Time Allowed : Three hours

Maximum Marks : 80

Minimum Pass Marks : 28

Note : Attempt all questions. Part (a) of each question is compulsory. Attempt any two parts from (b), (c) and (d) each question. Colors are allowed to make stick diagram and layout.

Unit-I

1. (a) What is Moore's Law? 2
- (b) Explain VLSI design flow. 7

328654(28)

PTO

[2]

- (c) Explain the switching characteristics of CMOS inverter. 7
- (d) Explain Transmission gate. Design Multiplexer with transmission gate. 7

Unit-II

- 2. (a) What is Lithography? 2
- (b) What are the fabrication processes for *n*-well CMOS? 7
- (c) Draw layout and stick diagram of 2 input NOR gate. 7
- (d) Explain Euler Graph with an example. 7

Unit-III

- 3. (a) What are SRAM and DRAM? 2
- (b) Draw layout of SR-Flip Flop. 7
- (c) Draw schematic and layout of multiplexer. 7
- (d) Explain the working of a 4×4 NOR based ROM array and draw its layout. 7

[3]

Unit-IV

- 4. (a) Define PAL and PLA. 2
- (b) Compare VLSI design style with FPGA and CPLD. 7
- (c) Explain concurrent and sequential signal Assignment with an example. 7
- (d) Write a VHDL code for Encoder. 7

Unit-V

- 5. (a) What is sequential circuits? 2
- (b) Write VHDL code to detect the sequence "101" using Moore State Machine. 7
- (c) Write VHDL code for D type Flip Flop with synchronous and asynchronous clear. 7
- (d) What is test bench synthesis? Explain with an example. 7