

333454(28)

**B. E. (Fourth Semester) Examination,
April-May 2020**

(New Scheme)

(IT Branch)

ANALOG ELECTRONICS CIRCUITS

Time Allowed : Three hours

Maximum Marks : 80

Minimum Pass Marks : 28

Note : Answer all questions. Part (a) is compulsory and carries 2 marks. Answer any two parts from (b), (c) and (d) carries 7 marks.


Unit - I

1. (a) What are the limitations of h-parameter model? 2
- (b) Analyse a transistor amplifier circuit using h-

[2]

parameters and derive the expression for A_p , R_p , R_o , A_v , A_{vs} , A_{IS} .

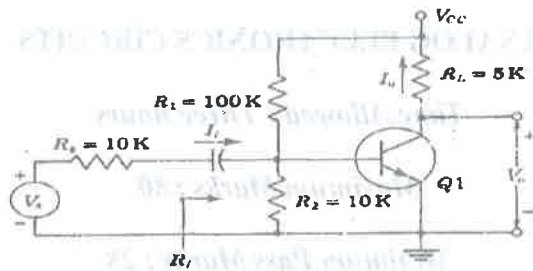- (c) State and prove the Miller's theorem and dual of Miller's theorem.
- (d) For the circuit shown, calculate $A_i = I_o/I_i$, A_v , A_{vs} , R_i and R_o . Transistor h parameters are as follows $h_{je} = 1.1 \text{ K}$, $h_{re} = 2.5 \times 10^{-4}$, $h_{fe} = 50$, $h_{oe} = 25 \mu \text{ A/V}$.



Unit - II

2. (a) What is the criteria for validity of h-pi-parameter?
- (b) Derive the expression for CE short circuit current gain A_i as a function of frequency.
- (c) Explain single stage CE transistor amplifier response at high frequency.

[3]

- (d) Given the following transistor measurements made at $I_C = 5 \text{ mA}$, $V_{CE} = 10 \text{ V}$, and at room temperature.

$h_{fe} = 100$, $h_{ie} = 600 \Omega$, $[A_{ie}] = 10$ at 10 MHz, $C_c = 3 \text{ pF}$. Find f_β , f_T , C_e , $r_{b'e}$, and $r_{b'c}$.

Unit - III

3. (a) What do you mean by fidelity of an amplifier?
- (b) Draw the two stages RC coupled amplifiers and explain its response at LF and HF.
- (c) Explain the effect of emitter bypass capacitor in low frequency response.
- (d) Explain different types of coupling amplifier.

Unit - IV

4. (a) Define desensitivity D.
- (b) Explain various topologies for negative feedback with their block diagrams.
- (c) What are the advantages and disadvantages of negative feedback?

- (d) Explain voltage series feedback with example. 7

Unit - V

5. (a) Differentiate between positive and negative feedback. 2
- (b) Explain Barkhausen Criterion and conditions of oscillation. 7
- (c) Explain RC phase shift oscillator and also derive the expression for cutout frequency. 7
- (d) Explain Colpitt's oscillator and also derive the expression for cutout frequency. 7